

WPCA – AMEREN ESP SEMINAR


Understanding ESP Controls

By John Knapik




Efficiency vs. Specific Corona Power


KNOW WHERE YOUR ESP RUNS ON
THE CURVE

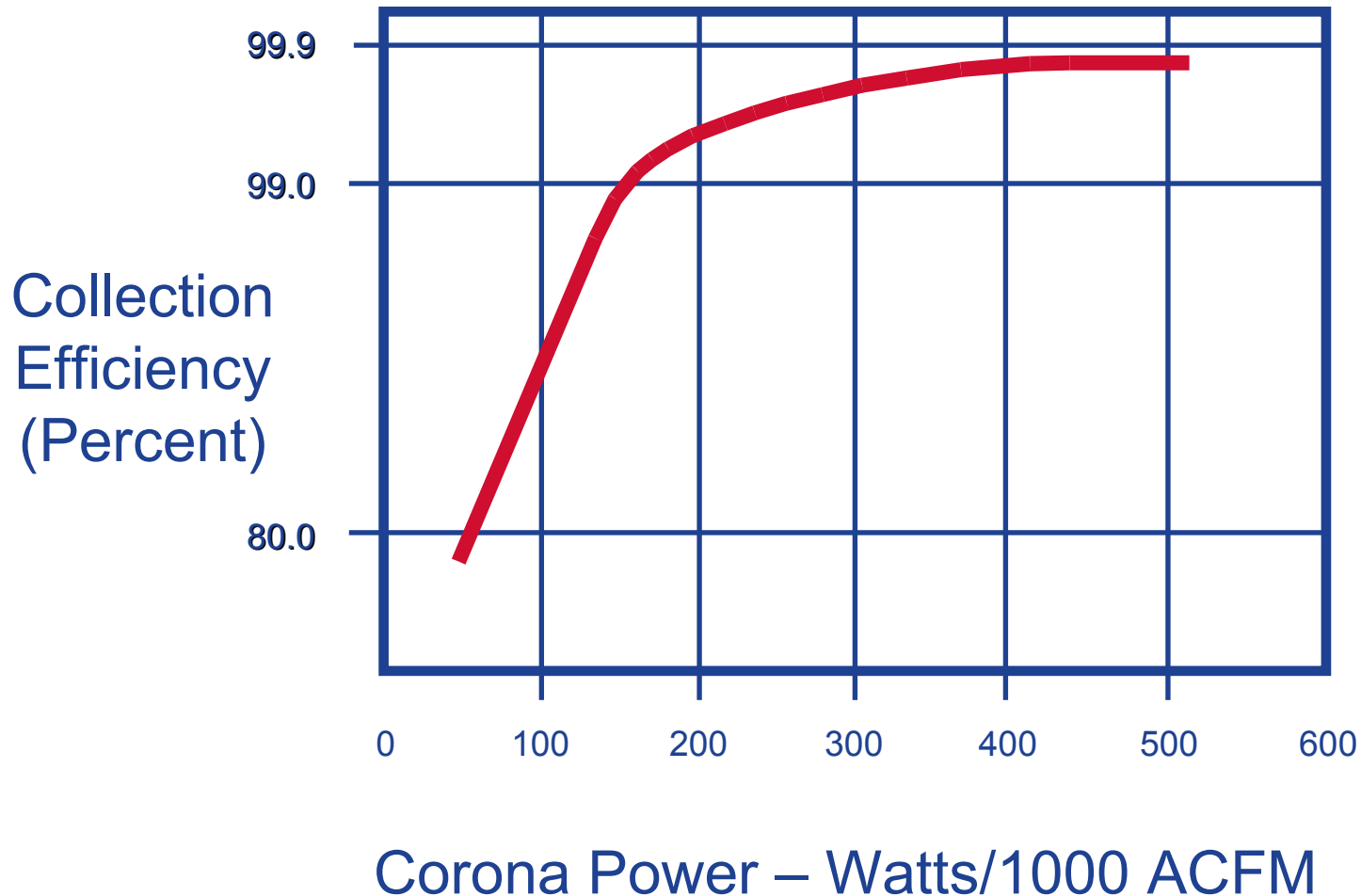

AVC Cabinet, CLR & T/R Set

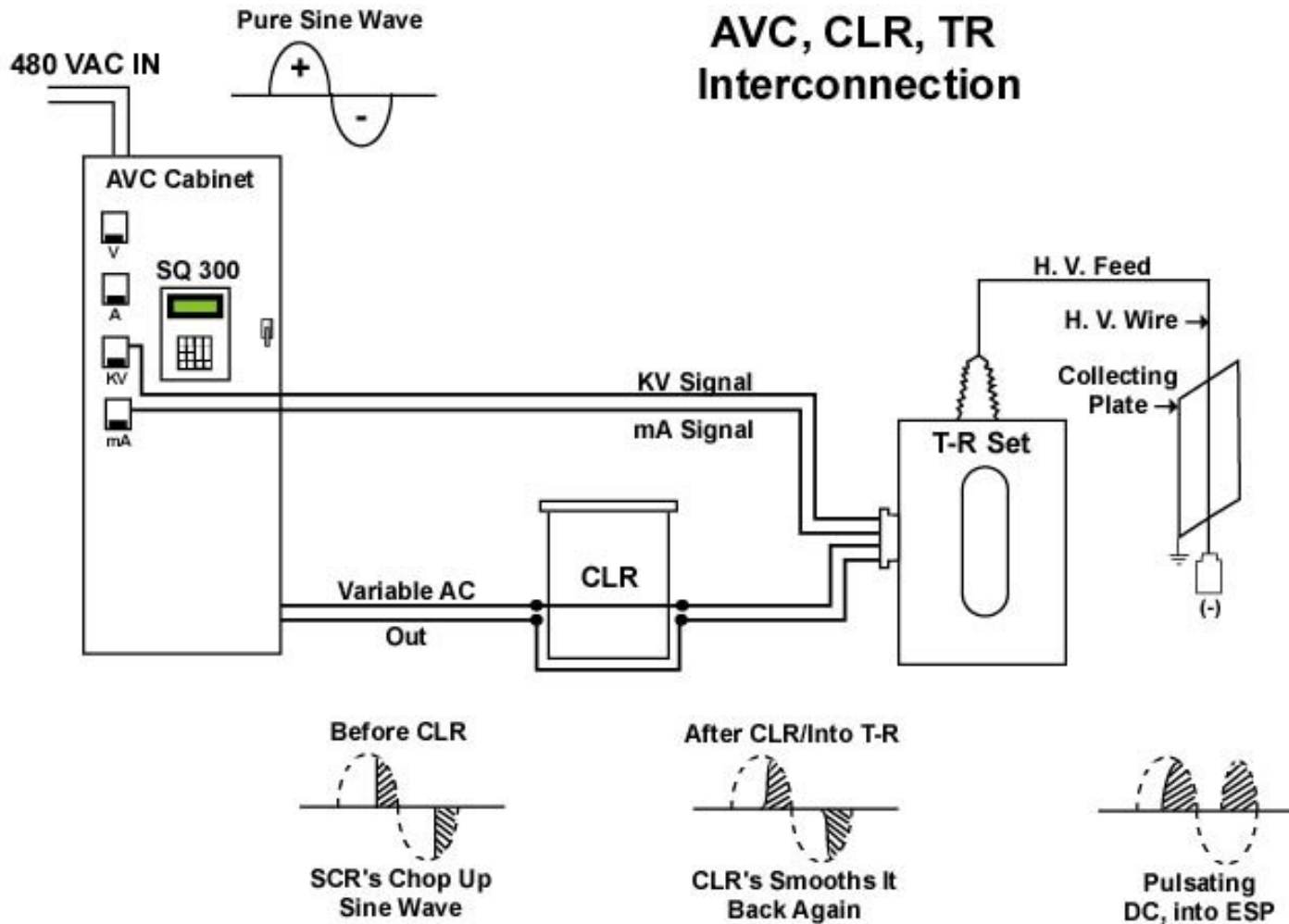

Typical SCR-CLR Electrical System

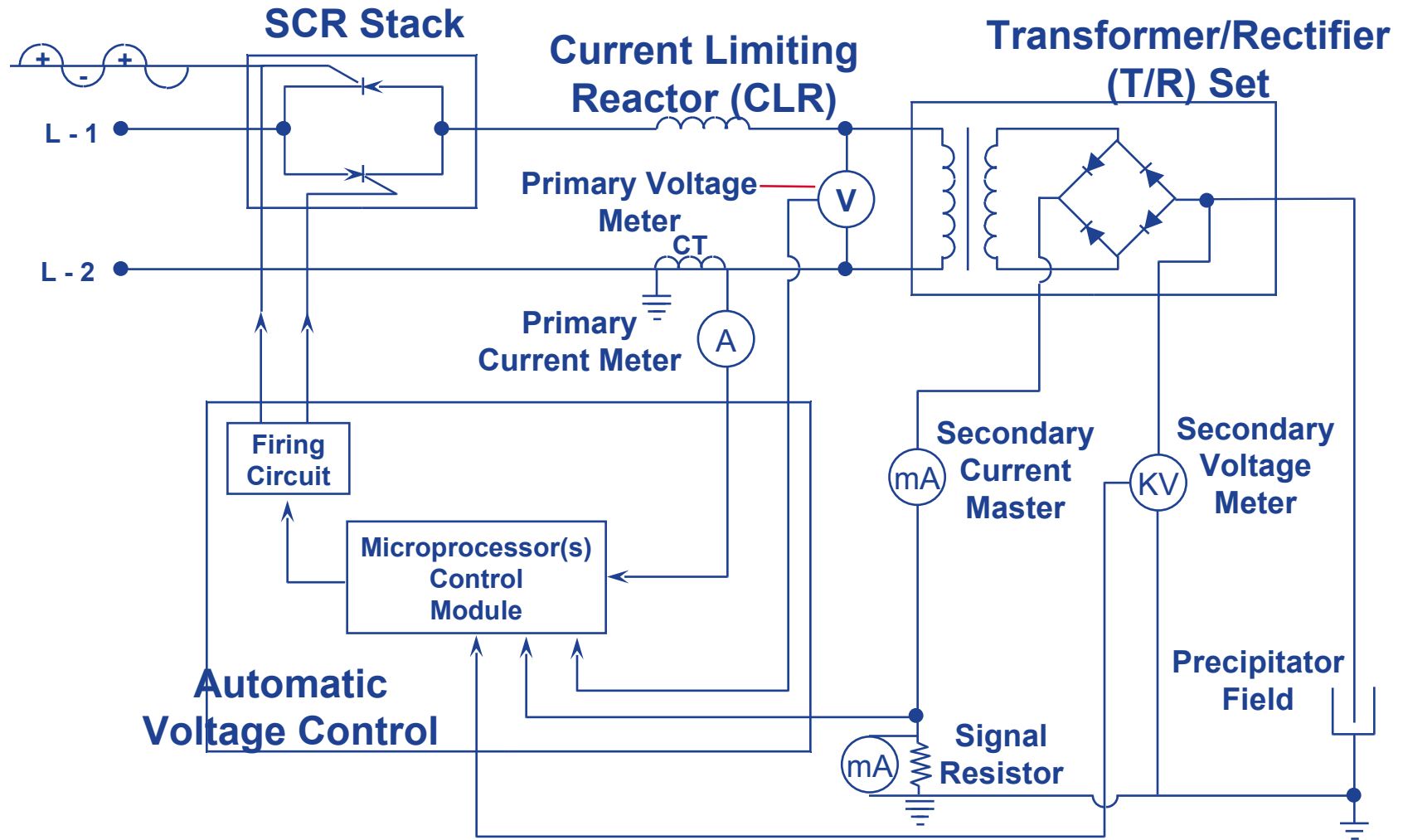

Just Remember, the Primary of a T-R Set is Rated in Units of RMS, the Secondary is in Average

- 400 V AC RMS
- 120 A AC RMS
- 45 KV DC Average
- 750 mA DC Average

Therefore use an RMS Reading Meter to Calibrate the Primary Meters

Note! How Do You Tell The Difference?




Iron Vane
Movement




D'Arsonval
Average

RMS
The Meter Scale Distance is not the Same on the RMS Meter.


Primary Current Meter

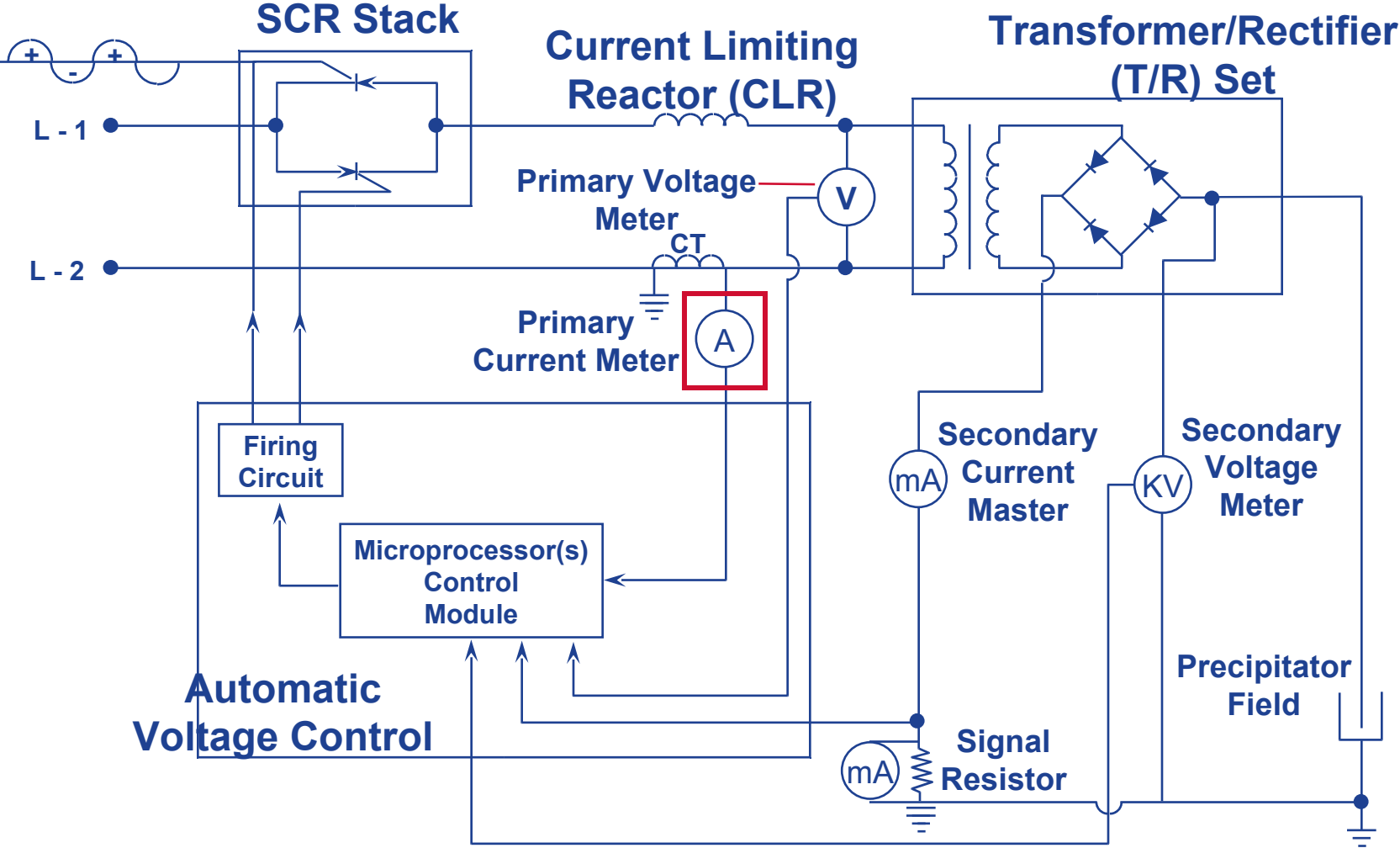

Finding the Primary Current Waveform

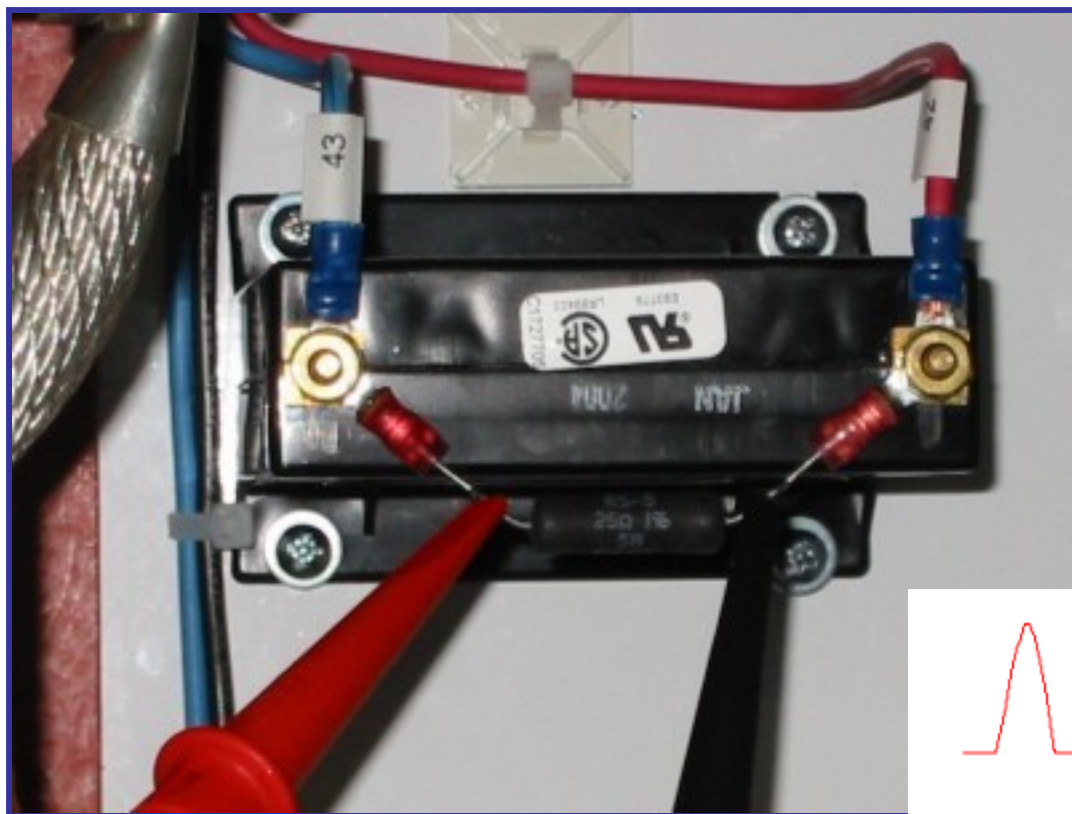


Primary Current – A Chopped Sine Wave

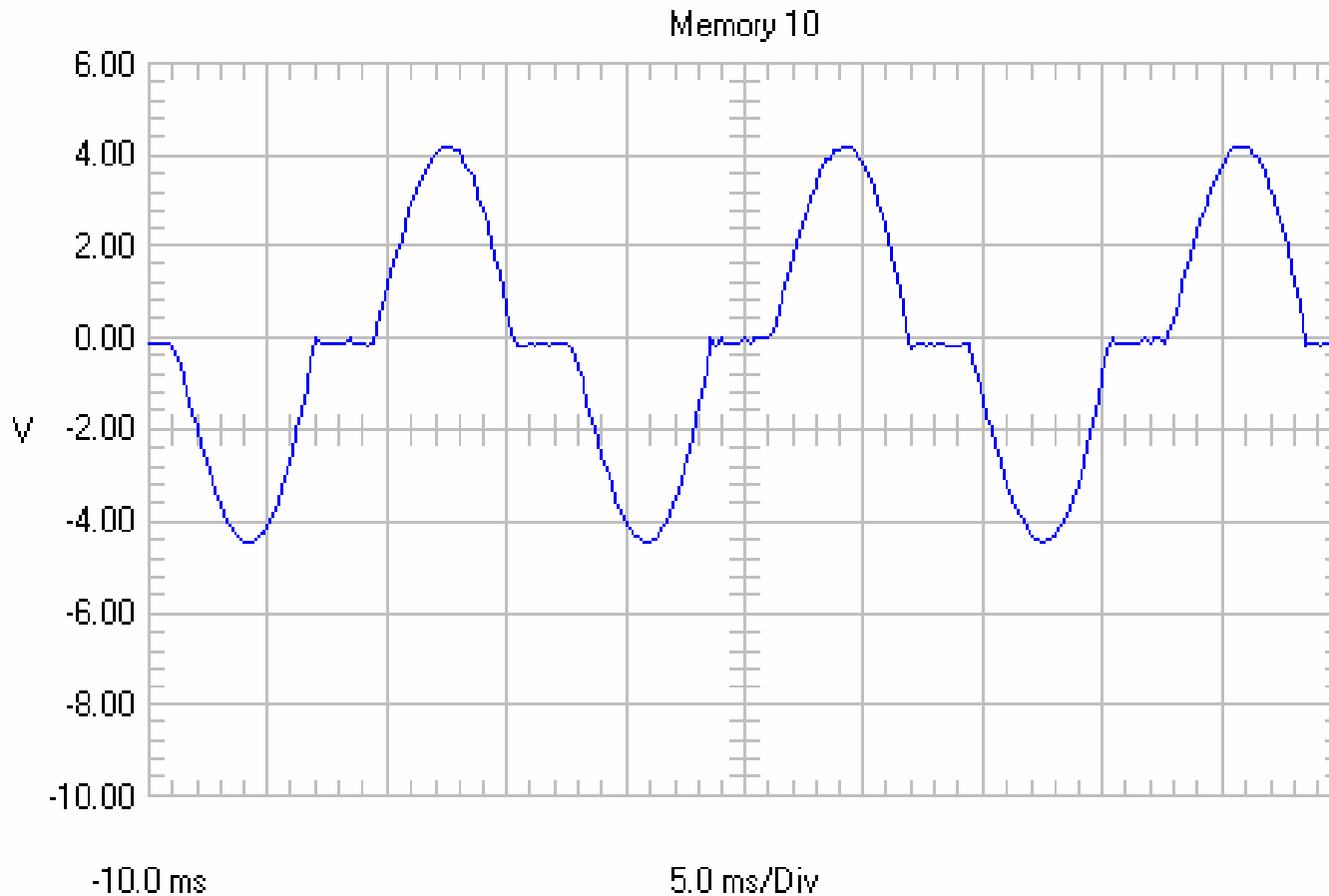


Datablock	
Name	= Memory 10
Date	= 12/4/97
Time	= 3:16:25 PM
Y Scale	= 2.00 V/Div
Y At 50%	= -2.00 V
X Scale	= 5.0 ms/Div
X At 0%	= -10.0 ms
X Size	= 250 (512)
Maximum	= 4.24 V
Minimum	= -4.48 V


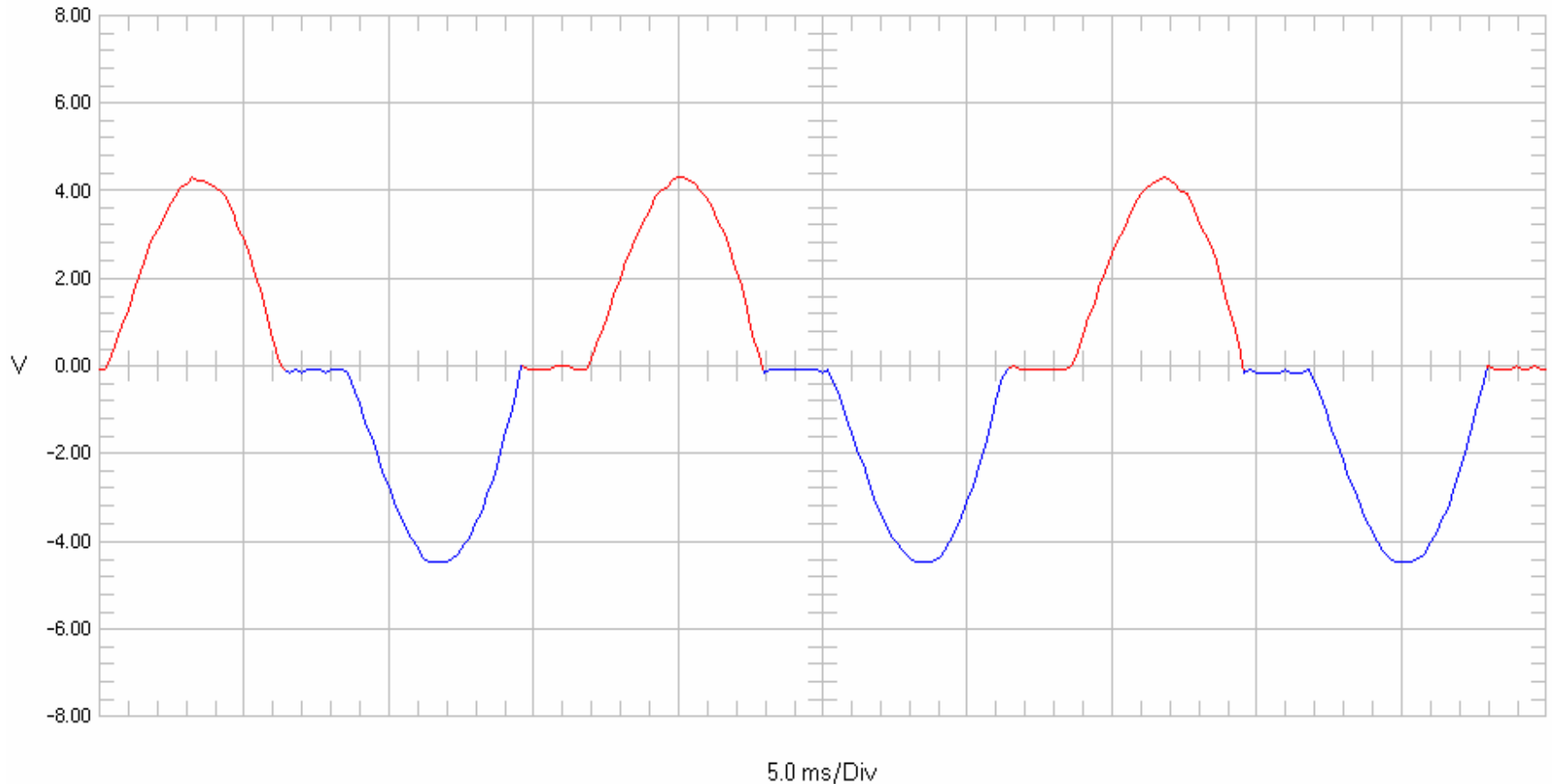
Primary Current Waveform - Positive and Negative Half-Cycles = SCR 1 and SCR 2




Secondary Current Meter

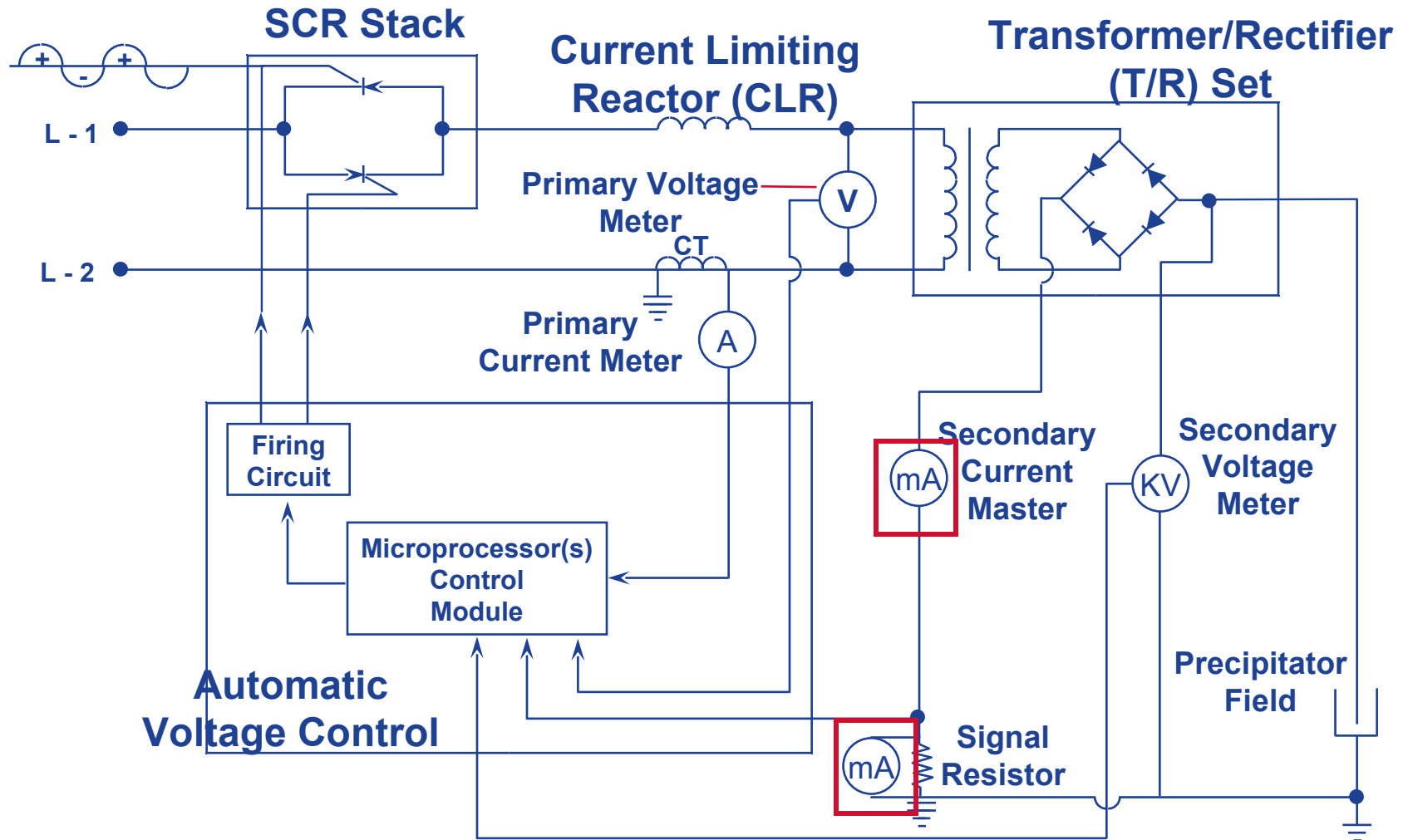

Finding the mA Signal

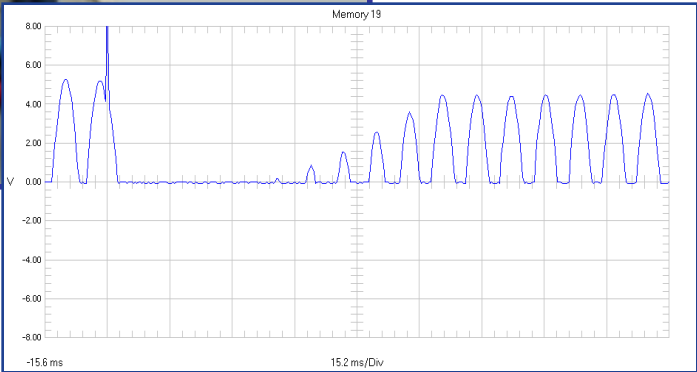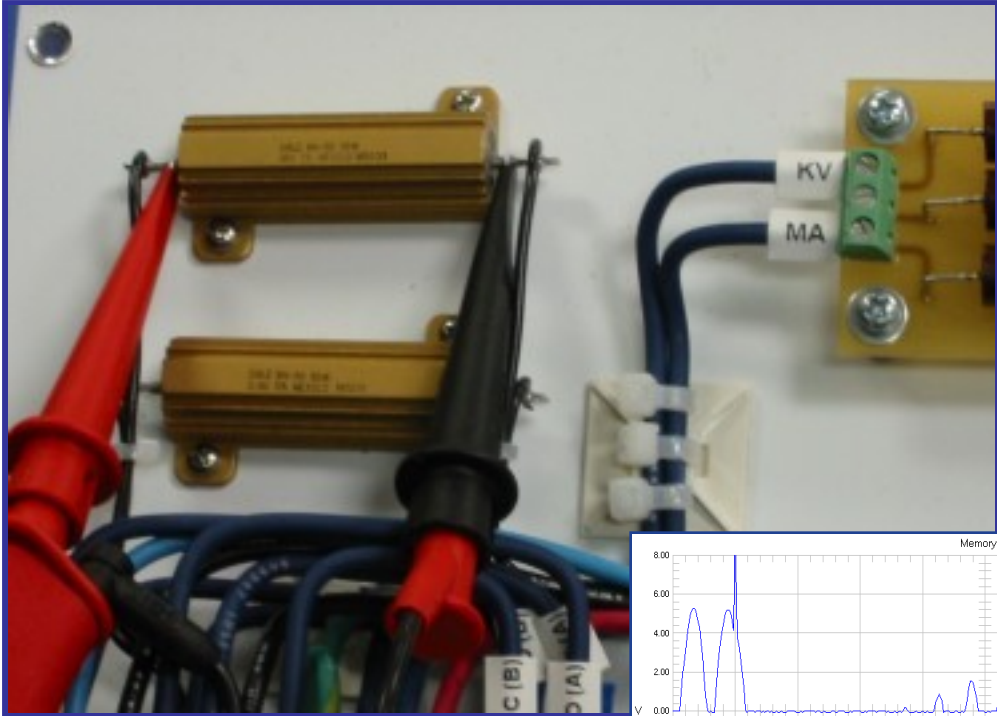


Secondary Current – Pulsating DC

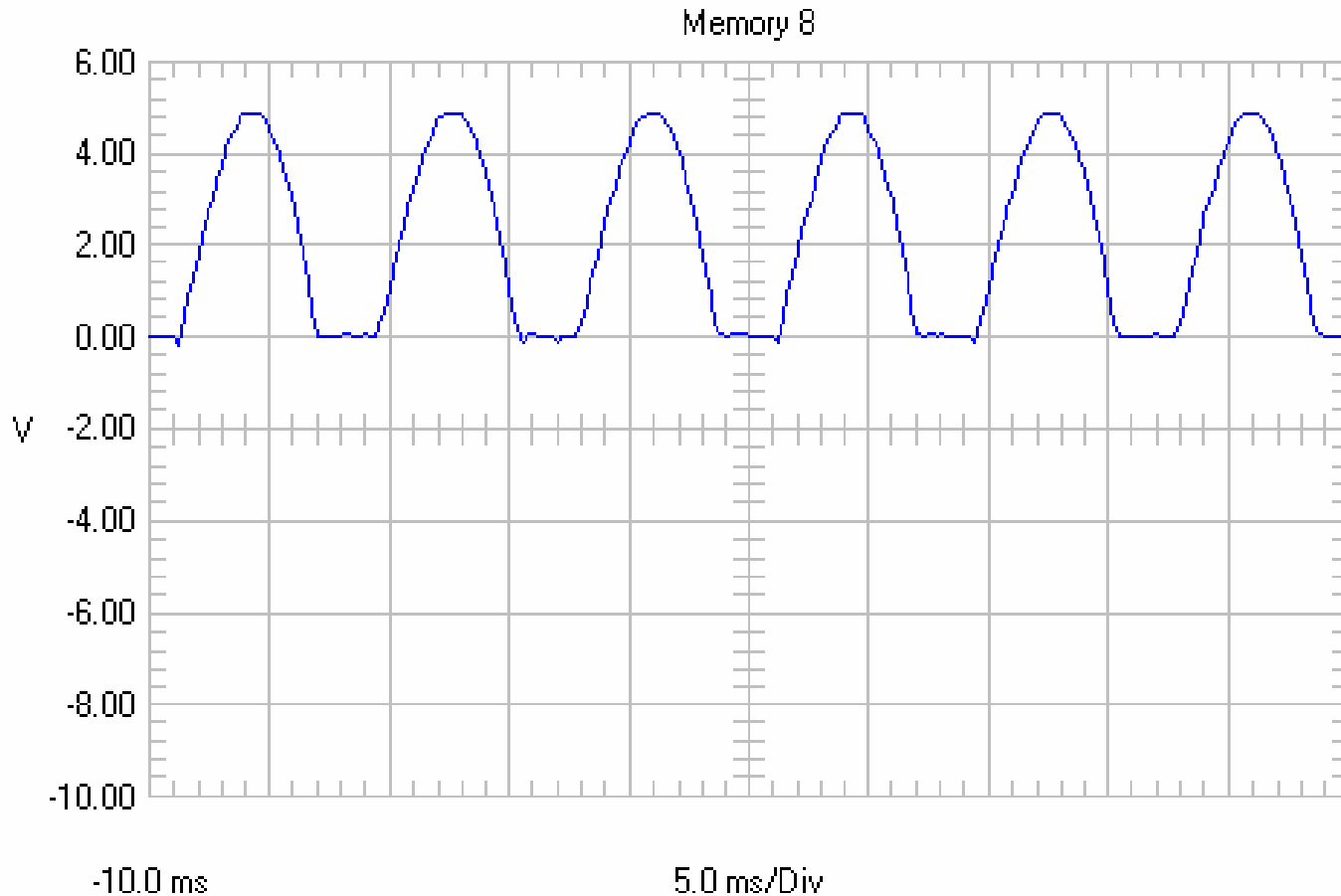


Datablock	
Name	= Memory 8
Date	= 12/4/97
Time	= 3:16:23 PM
Y Scale	= 2.00 V/Div
Y At 50%	= -2.00 V
X Scale	= 5.0 ms/Div
X At 0%	= -10.0 ms
X Size	= 250 (512)
Maximum	= 4.88 V
Minimum	= -0.16 V


Typical Primary and Secondary Current

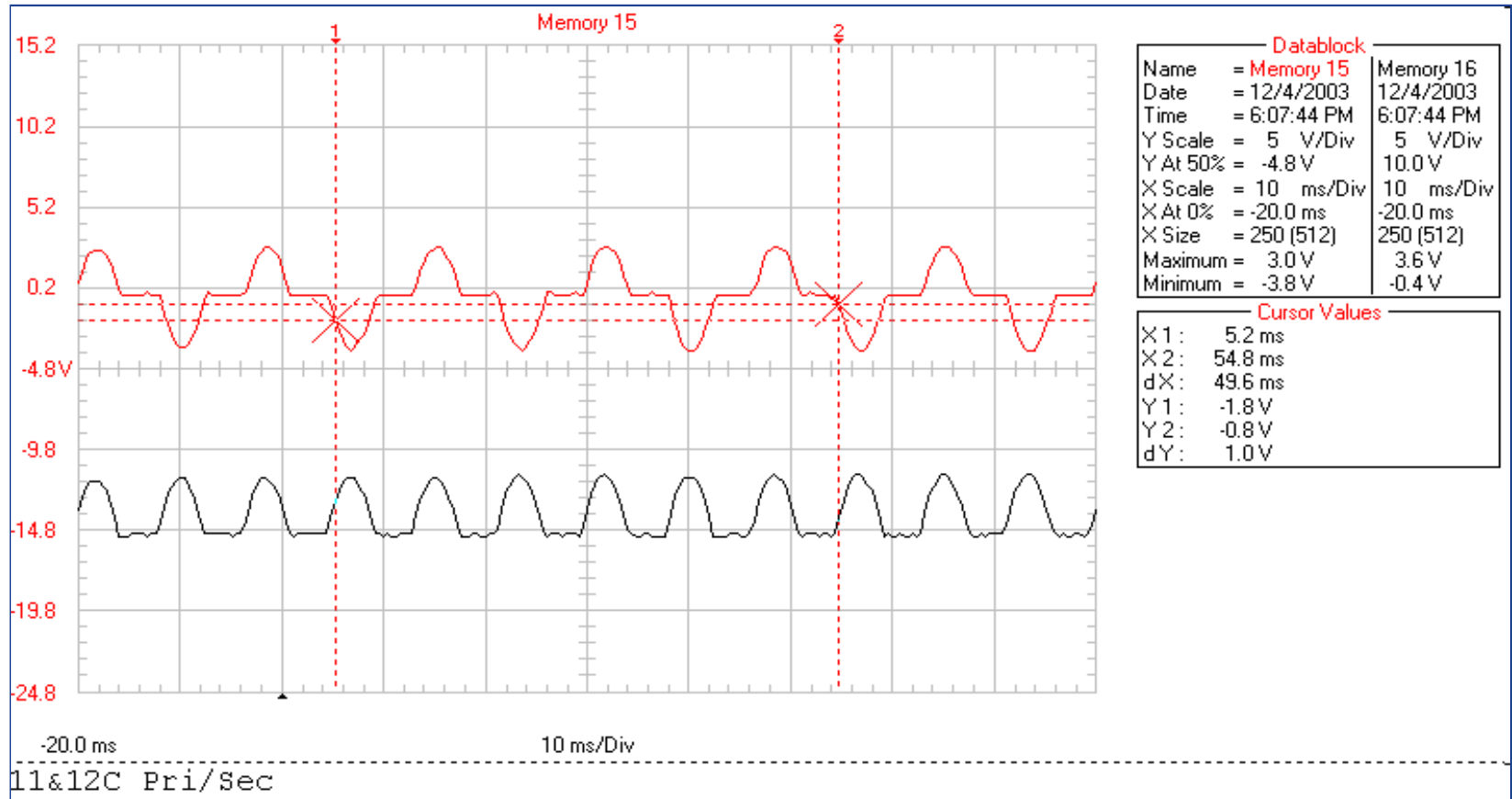


Secondary Voltage Meter

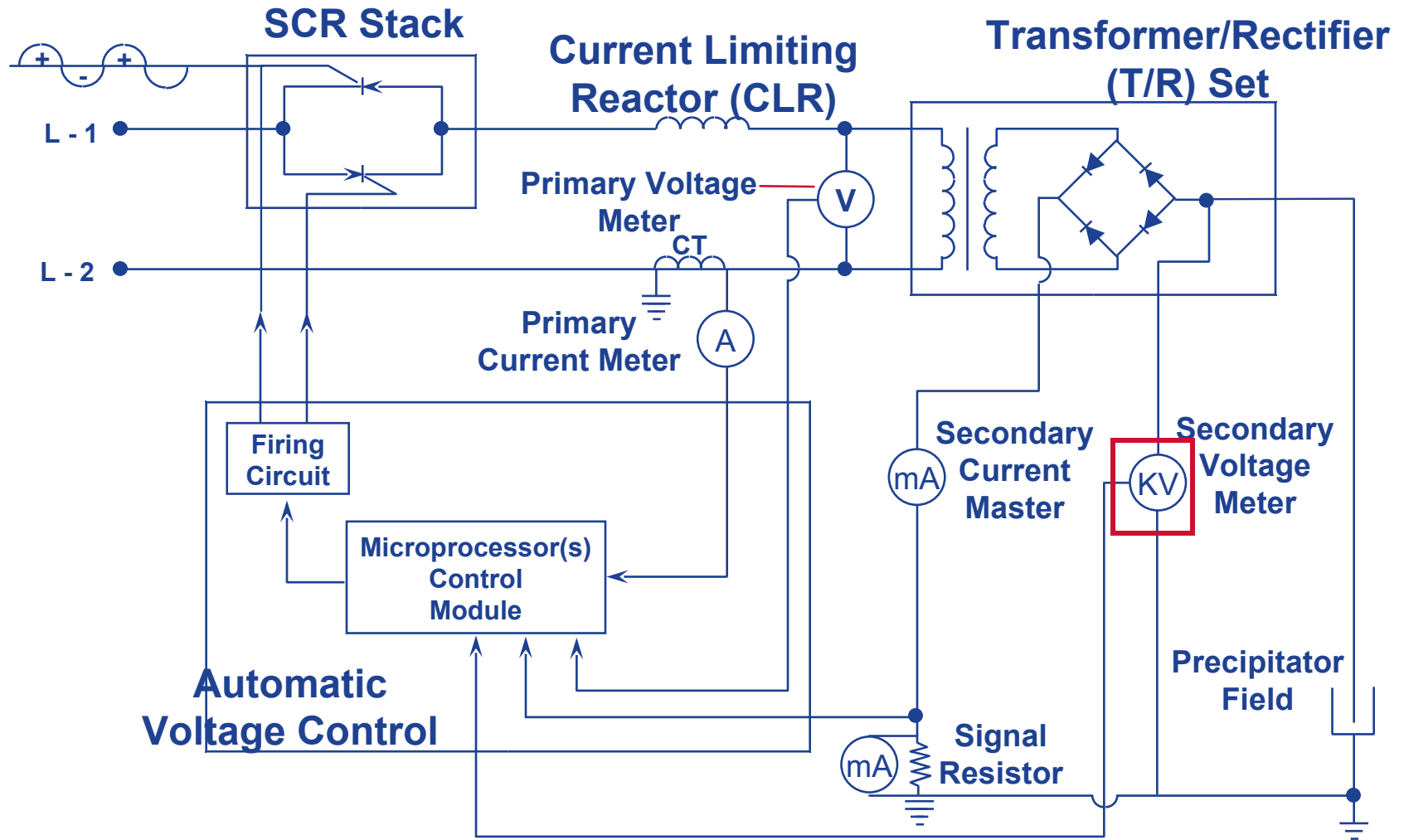


Current Limit - mA & KV

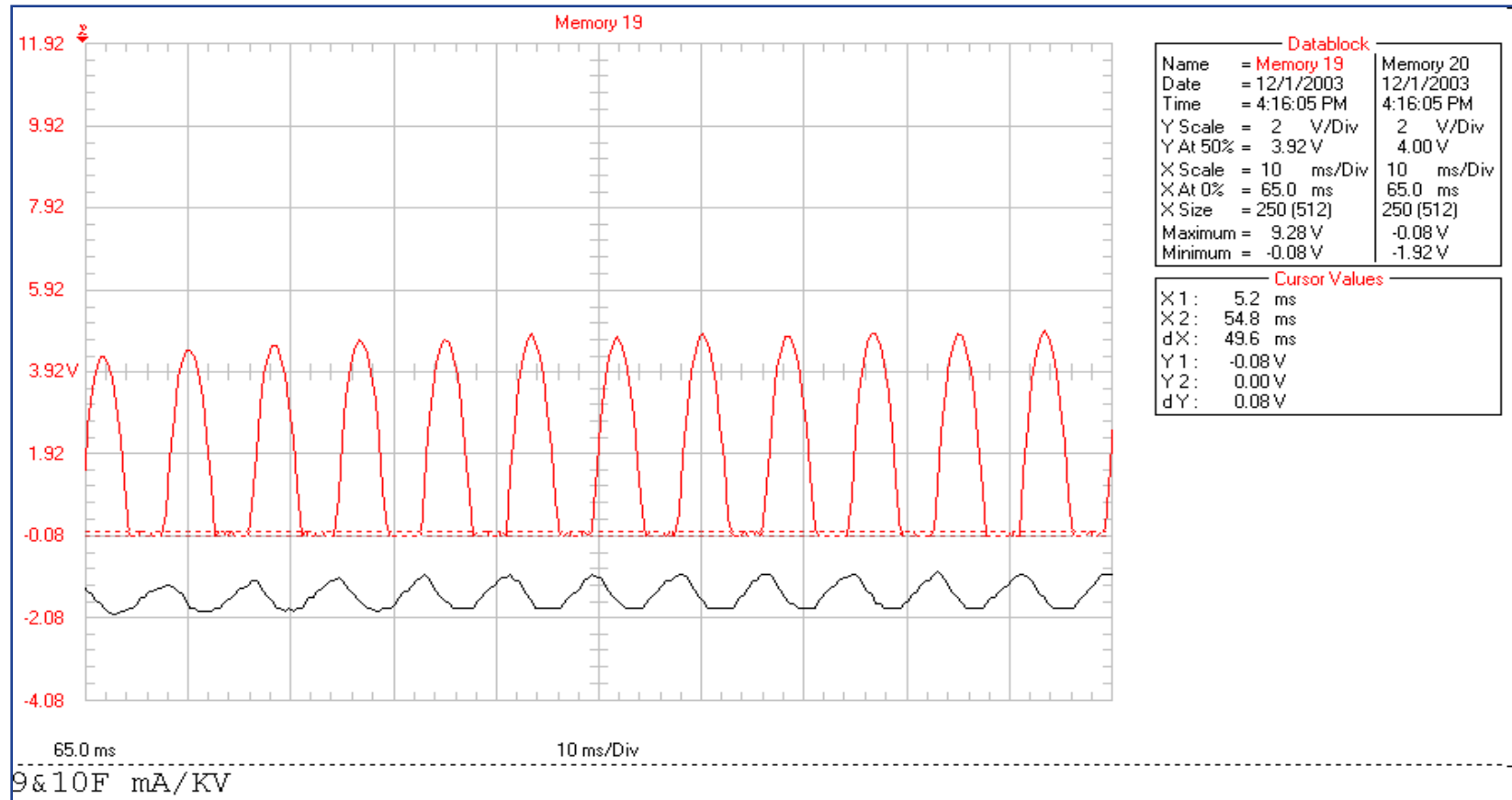

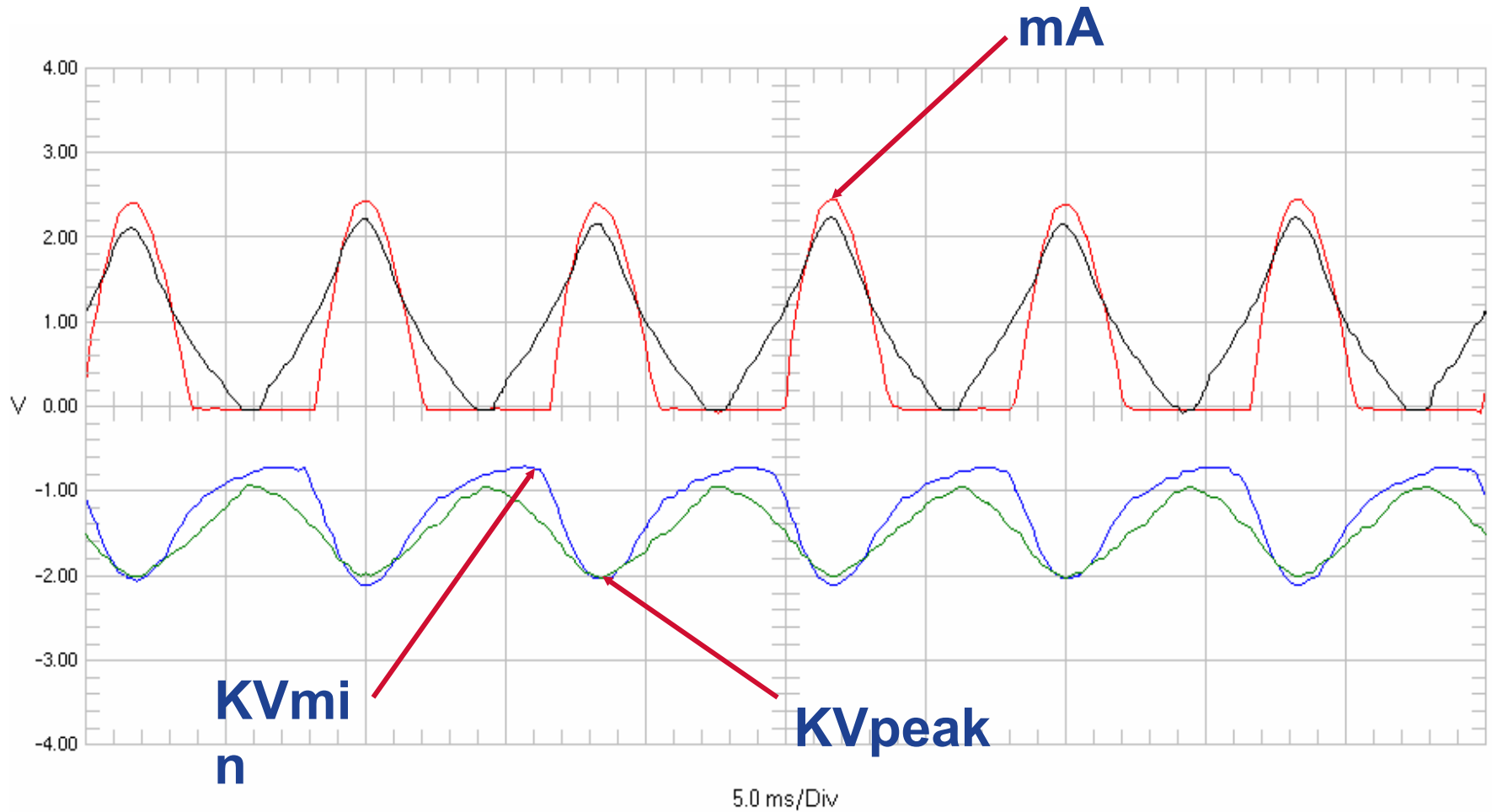Secondary Voltage Waveforms – True Negative



Next – The Automatic Voltage Control

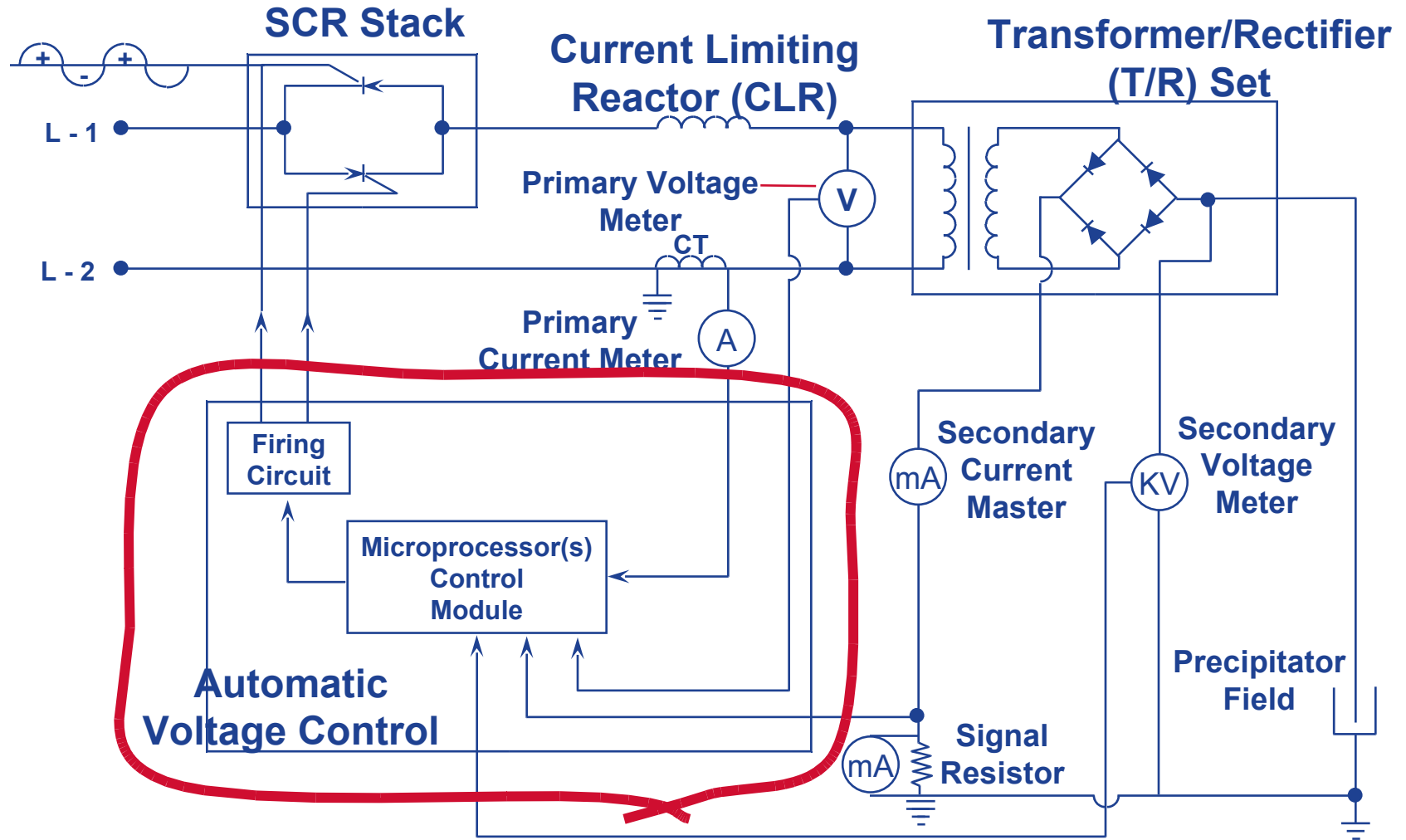

The **AVC**
is the **BRAINS**
of the ESP

Older Analog AVC



Microprocessor Based AVC




The AVC has 2 Jobs to Execute

- Control the amount of sparking in the ESP.
- If a T/R set is not sparking, then its AVC should be pushing that T/R set to one of its pre-set, healthy limits (volts, amps, KV, ma, or firing angle).
- I'll explain what is meant by "healthy" in a minute


The AVC has 2 Jobs to Execute...

But how does the AVC know
what's happening in the
ESP?


The mA signal is its eyes!

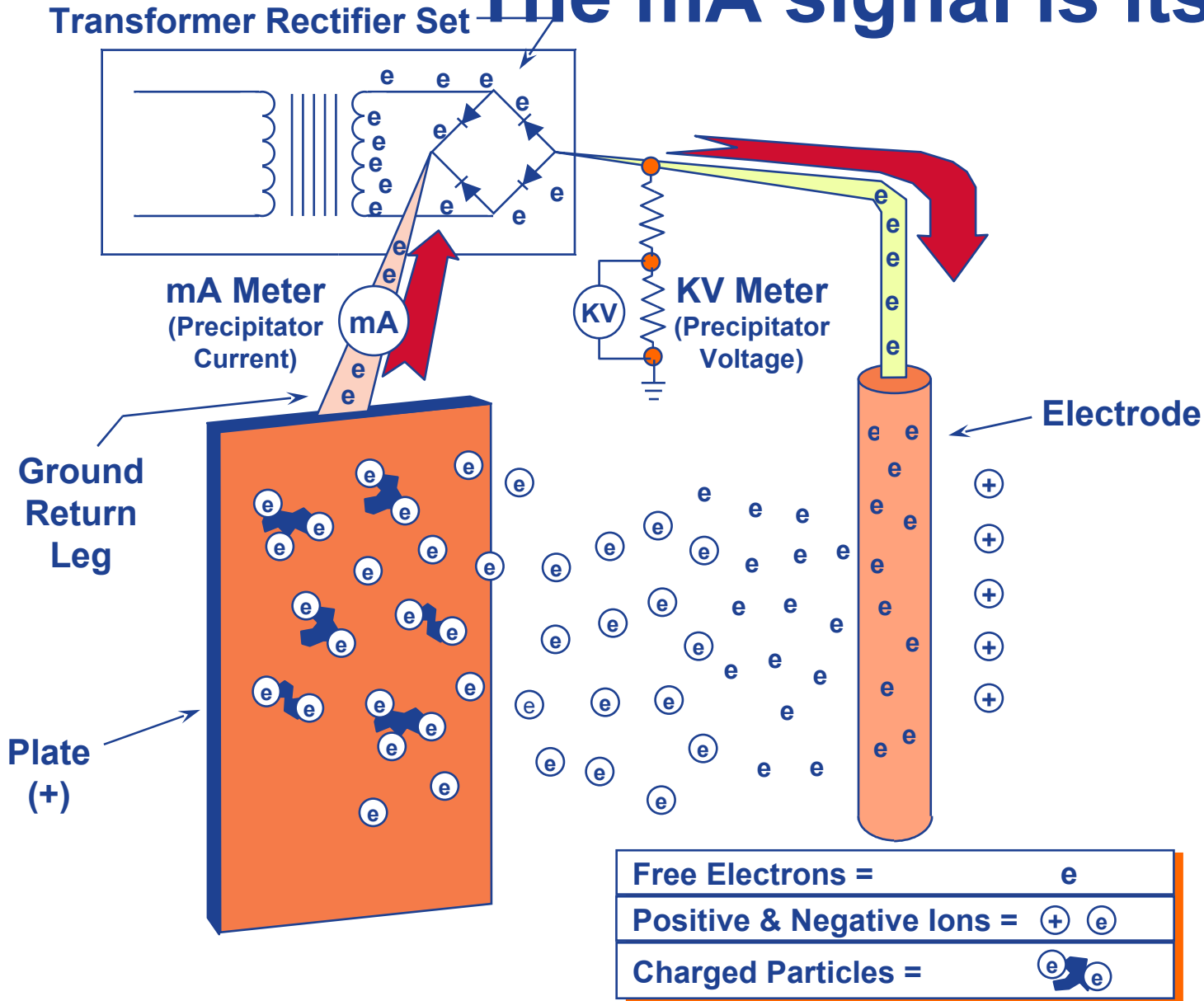

AVC Cabinet, CLR & T/R Set

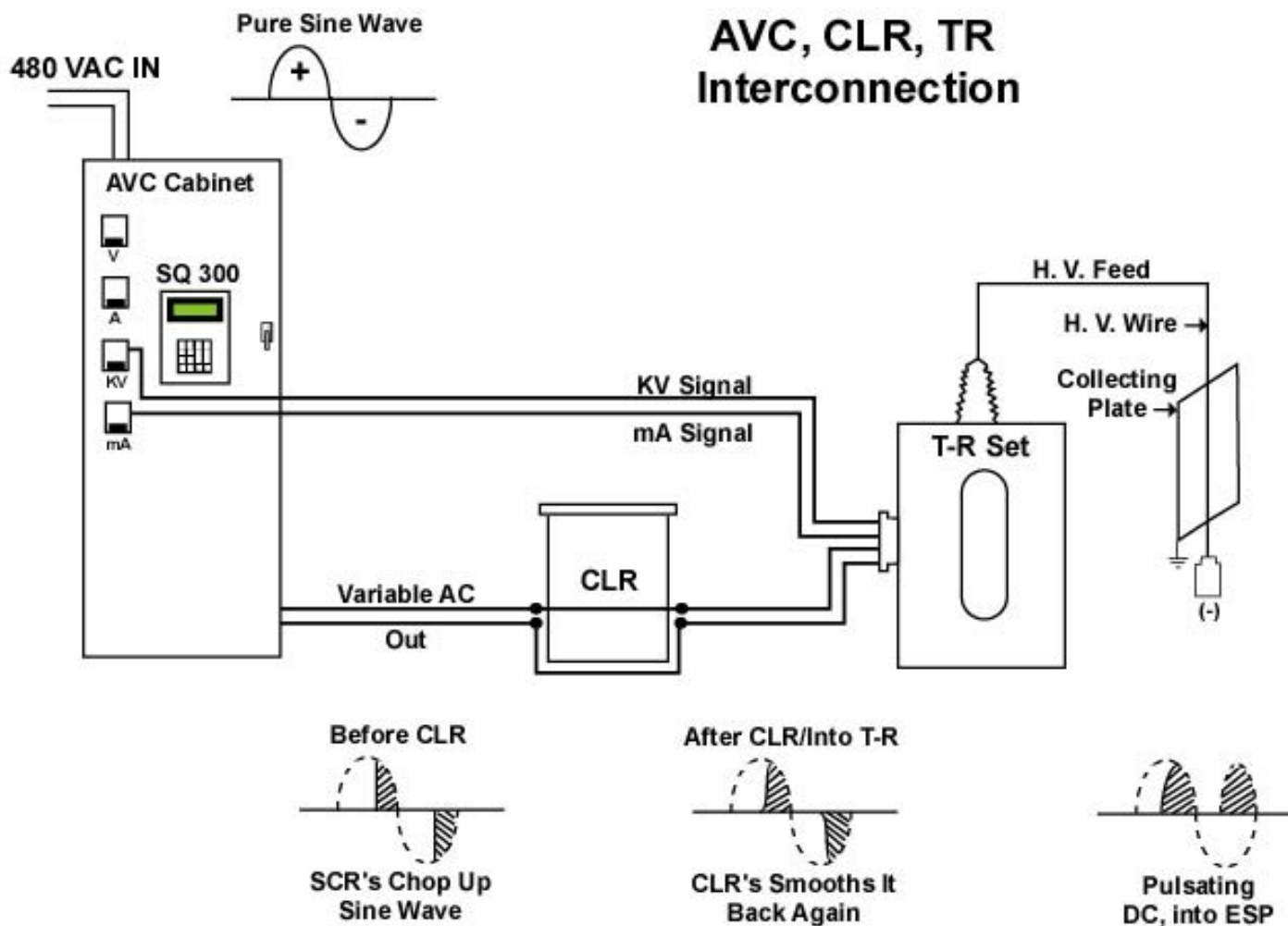


AVC Spark Response

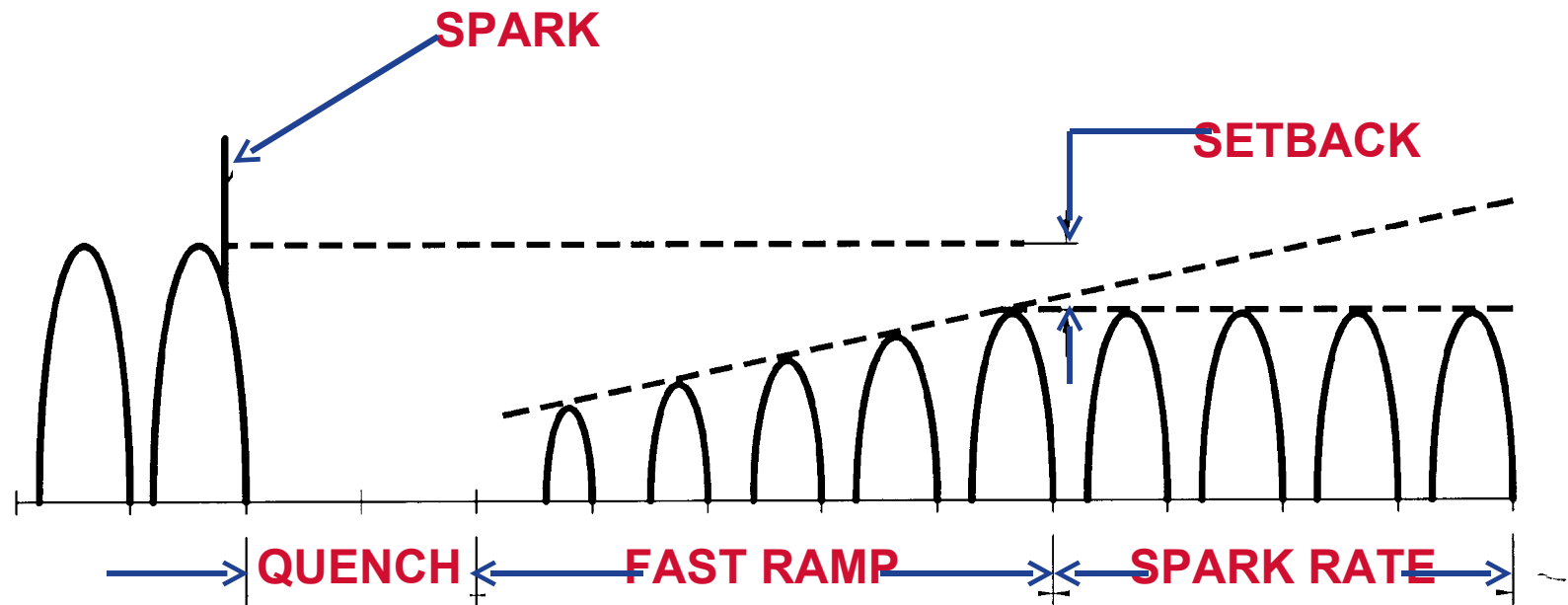


Good Initial Settings for an AVC

1. Quench = 1 Full Cycle
2. Fast Ramp = 5 or 6 Half Cycles
3. Setback = 15 to 20%
4. Spark Rate = 30SPM


Proper AVC Response to Sparking

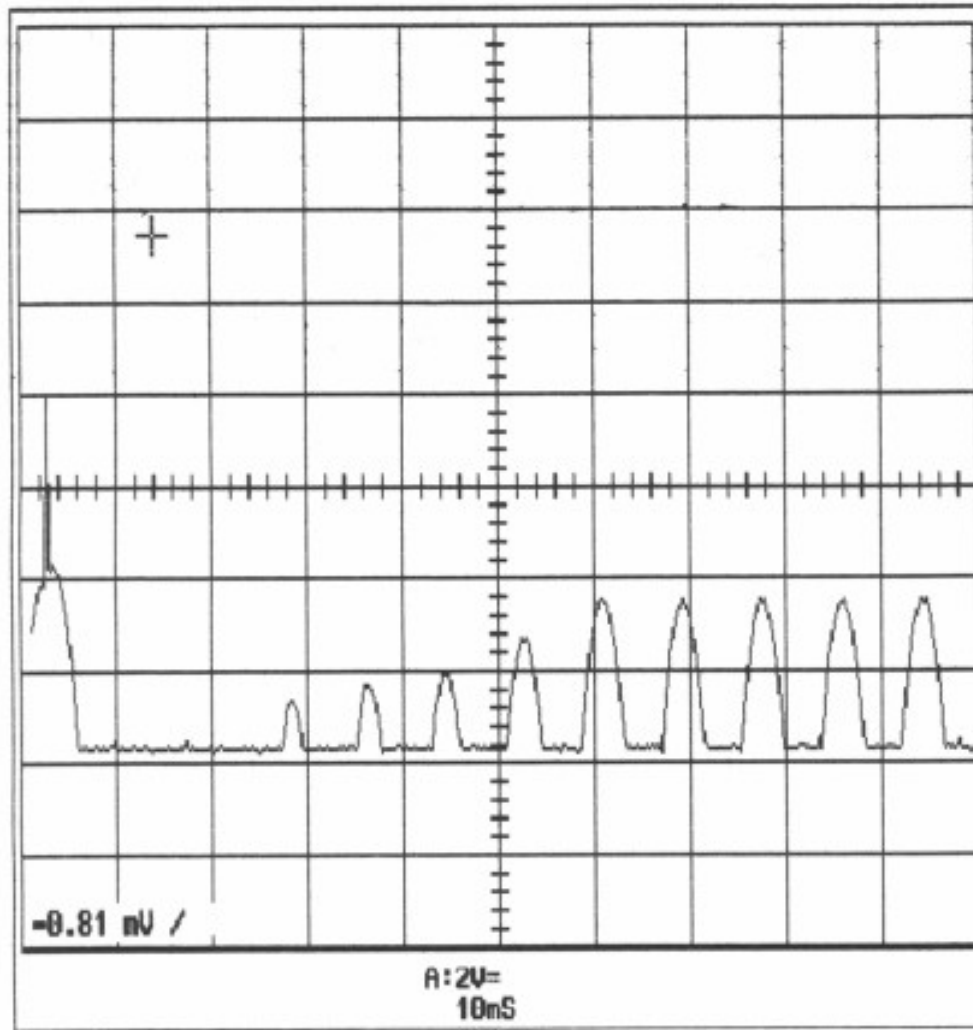

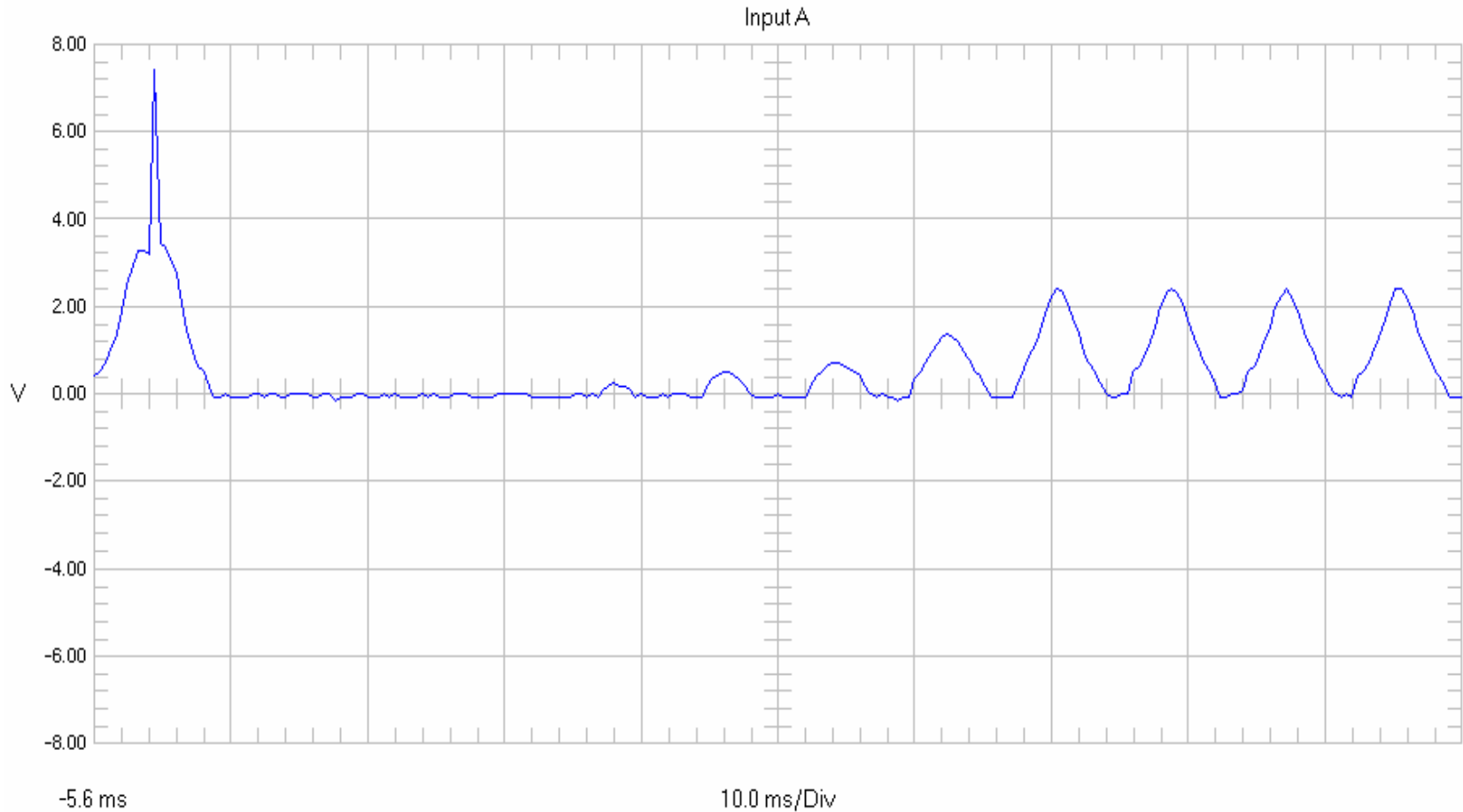
Spark Response - Secondary Current Waveform



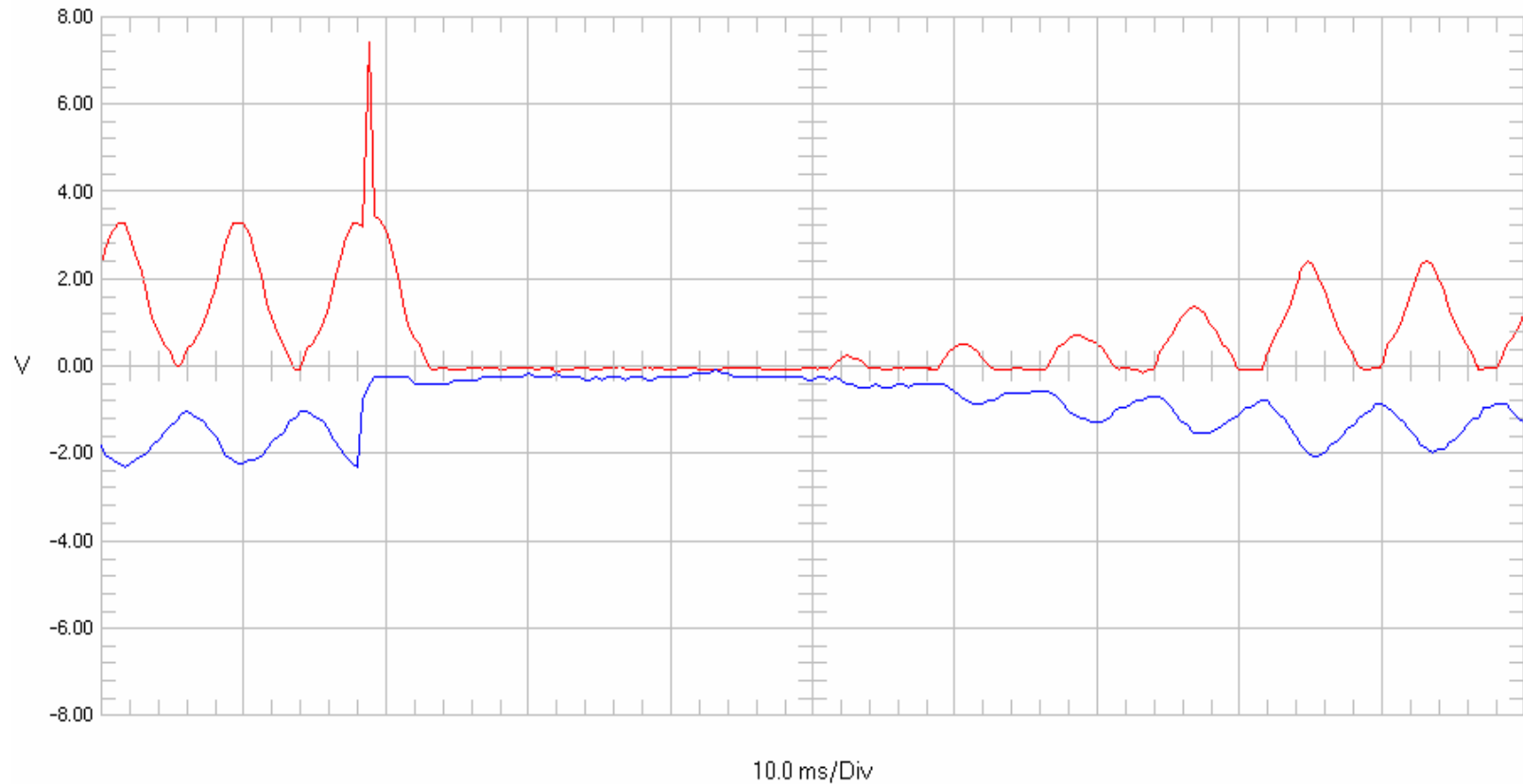
Spark Response - Secondary Current and Voltage Waveforms




Typical Spark Response - mA & KV

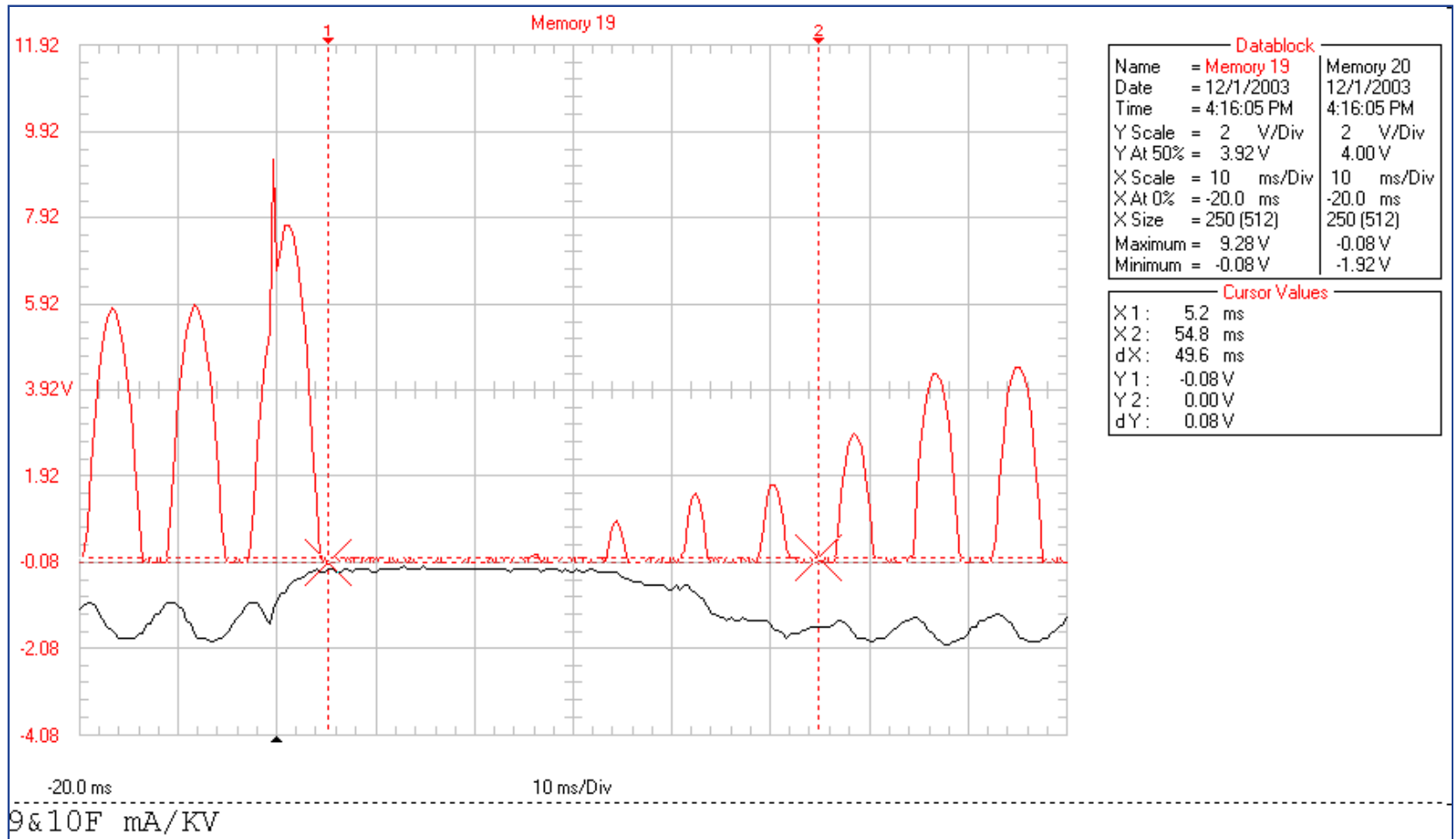


Further Control – A Search Ramp Rate

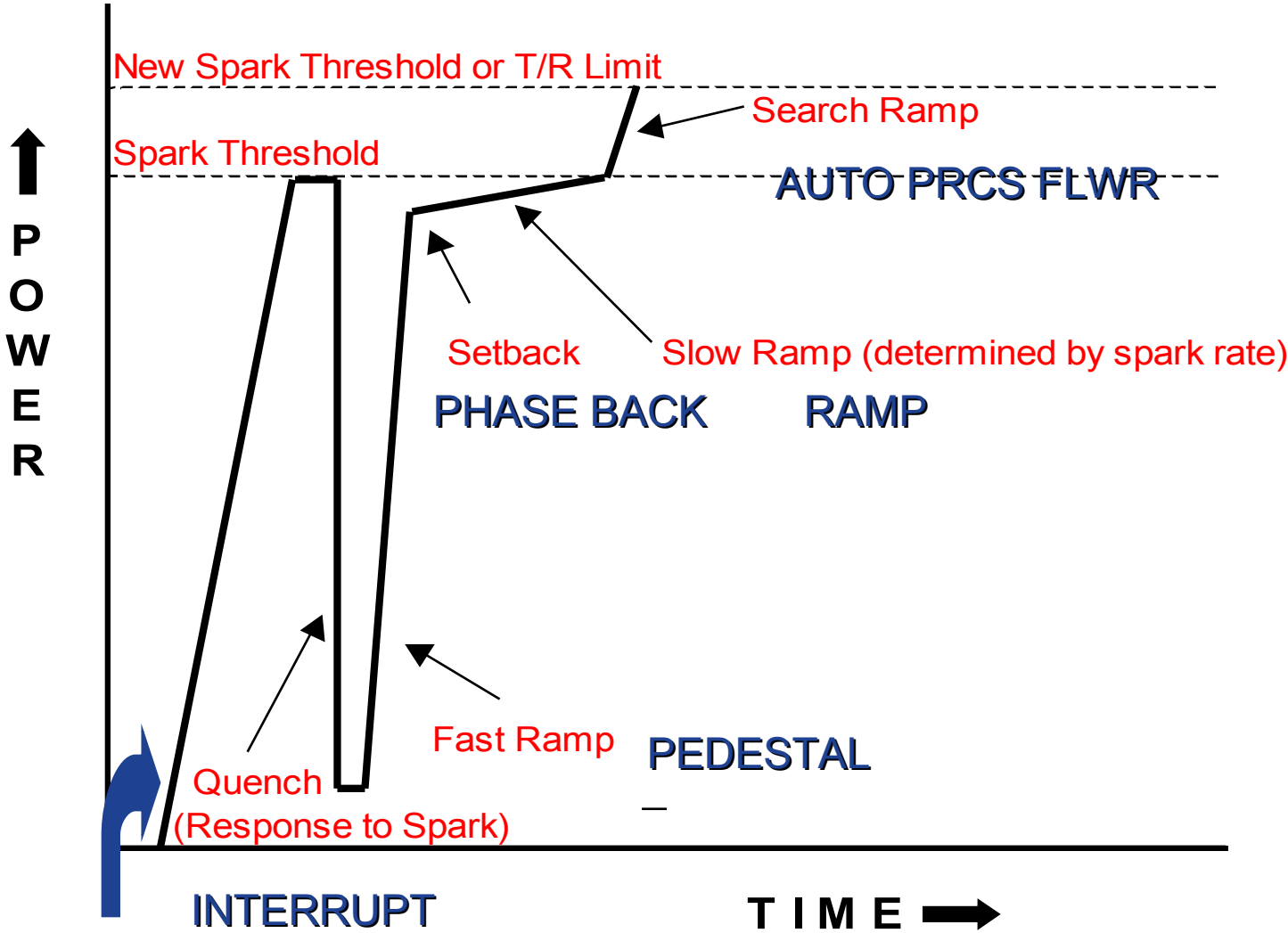

Spit Spark Response (mA)

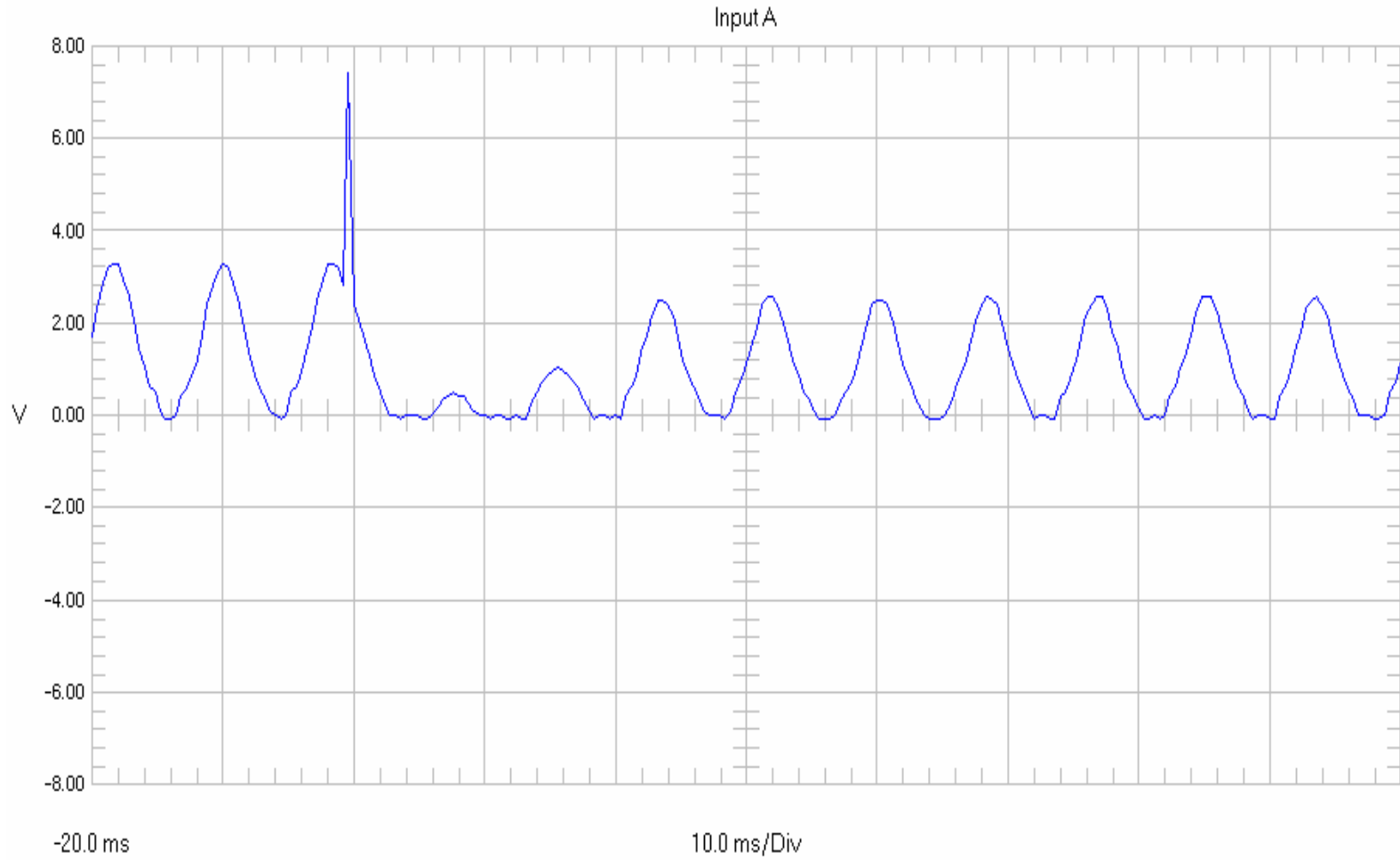

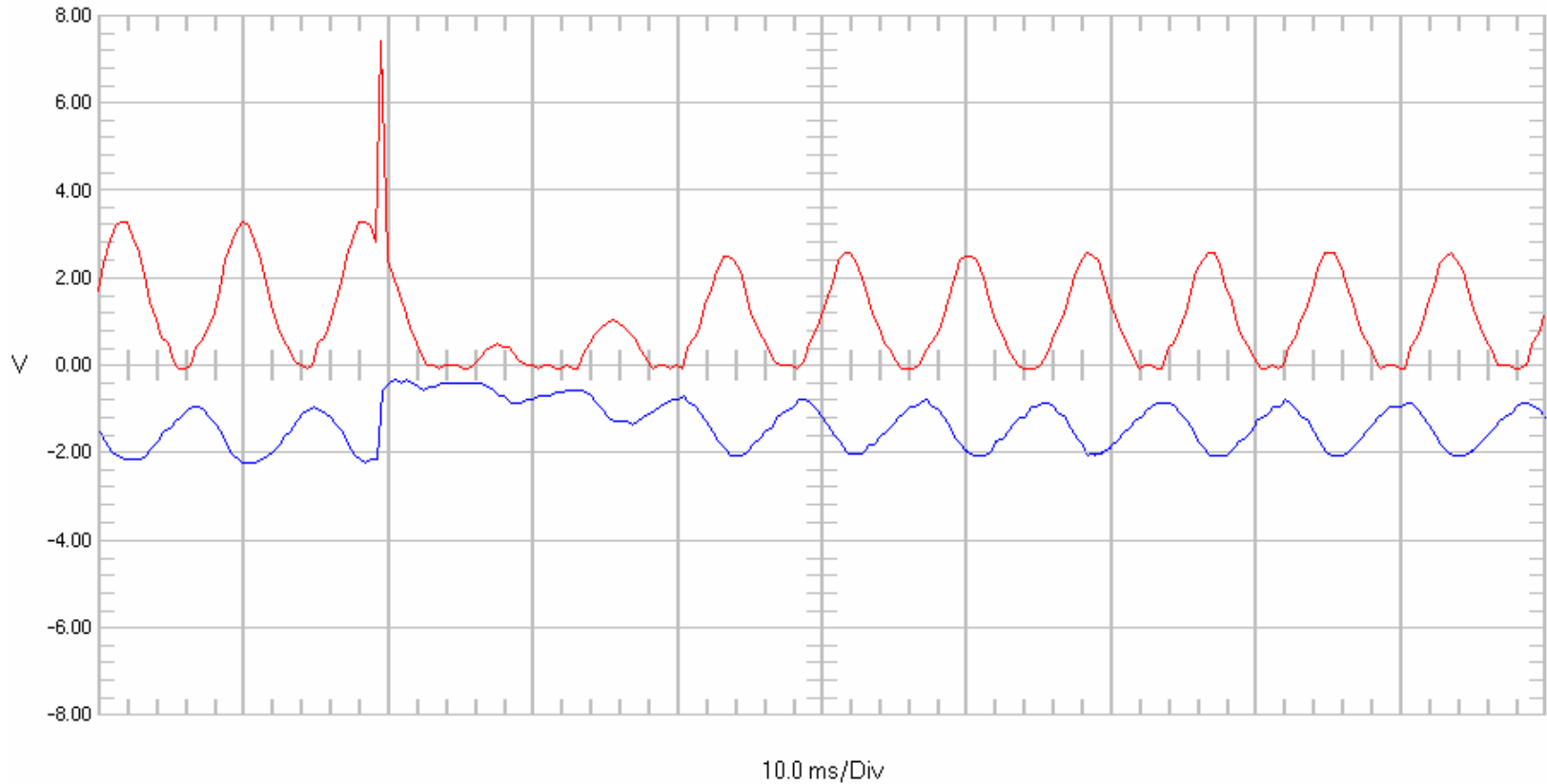Spit Spark Response - Secondary Current and Voltage Waveforms



Examples of AVC 's at a Limit



imagination at work


AVC SPARK LIMITED – DOING IT'S JOB



T/R Current Limited with Sparking



T-R CURRENT LIMITED WITHOUT SPARKING

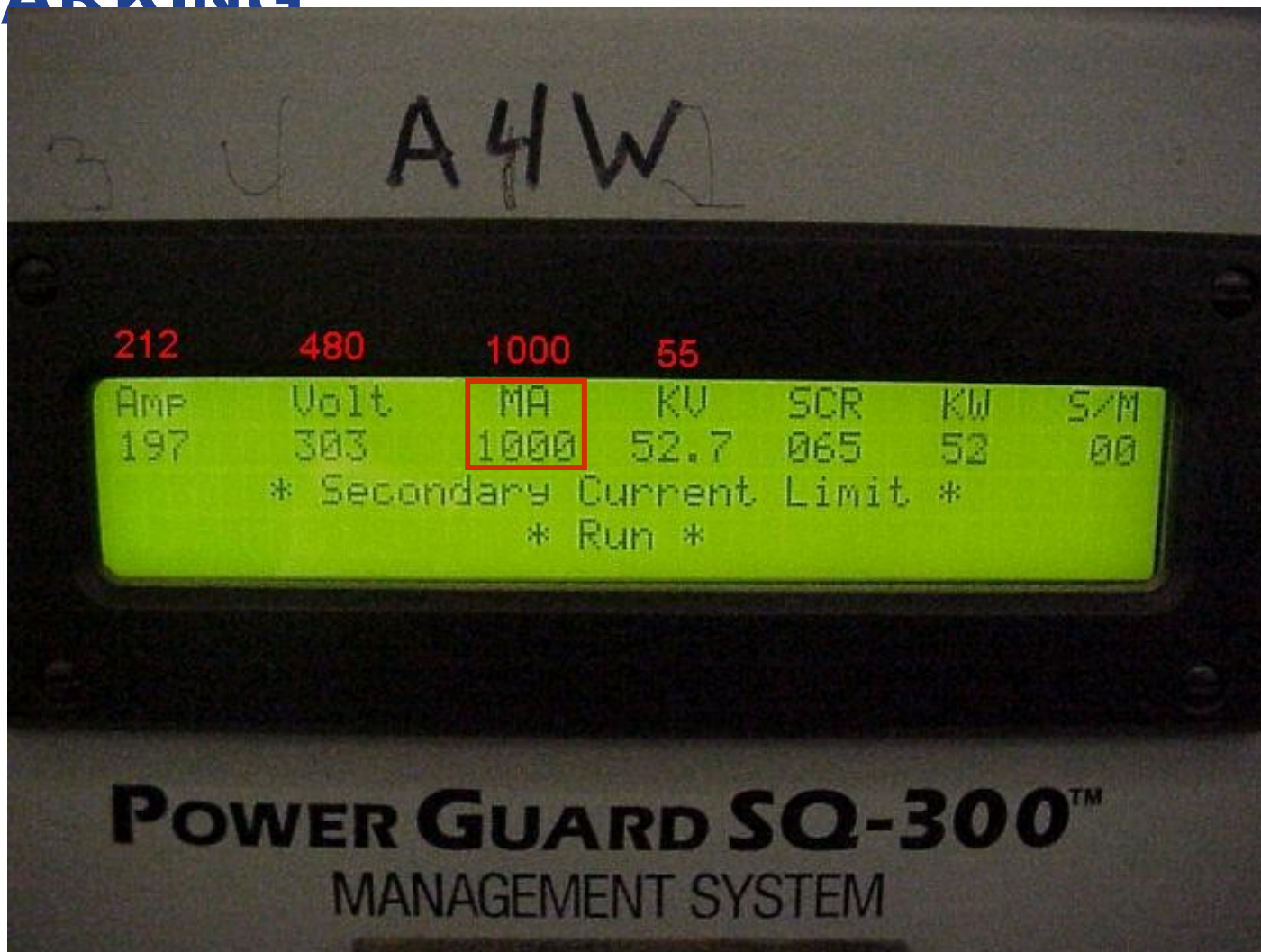


T-R VOLTAGE LIMITED WITH SPARKING



What is meant by “Healthy Limits?”

- Primary or Secondary Limit is not healthy when accompanied by a Primary Voltage level < 90 VAC or a Secondary level < 12 KV. It usually indicates a short circuit.
- Secondary Voltage Limit is not healthy when there is very little Secondary Current. It usually indicates an open circuit.
- Neither condition is aiding in particle capture


The T-R Set

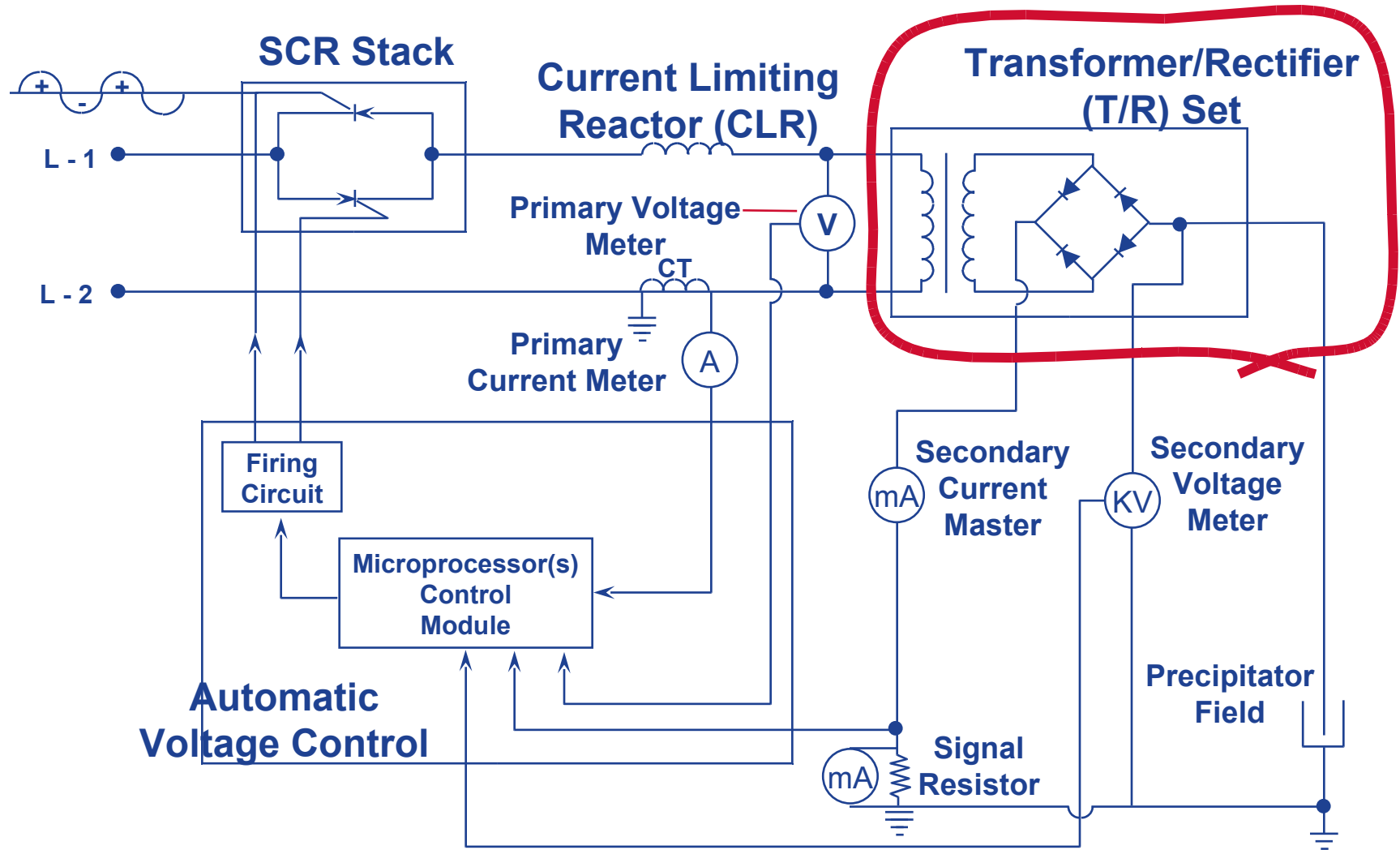

Transformer Rectifier (T/R) Set



Inside T/R Tank

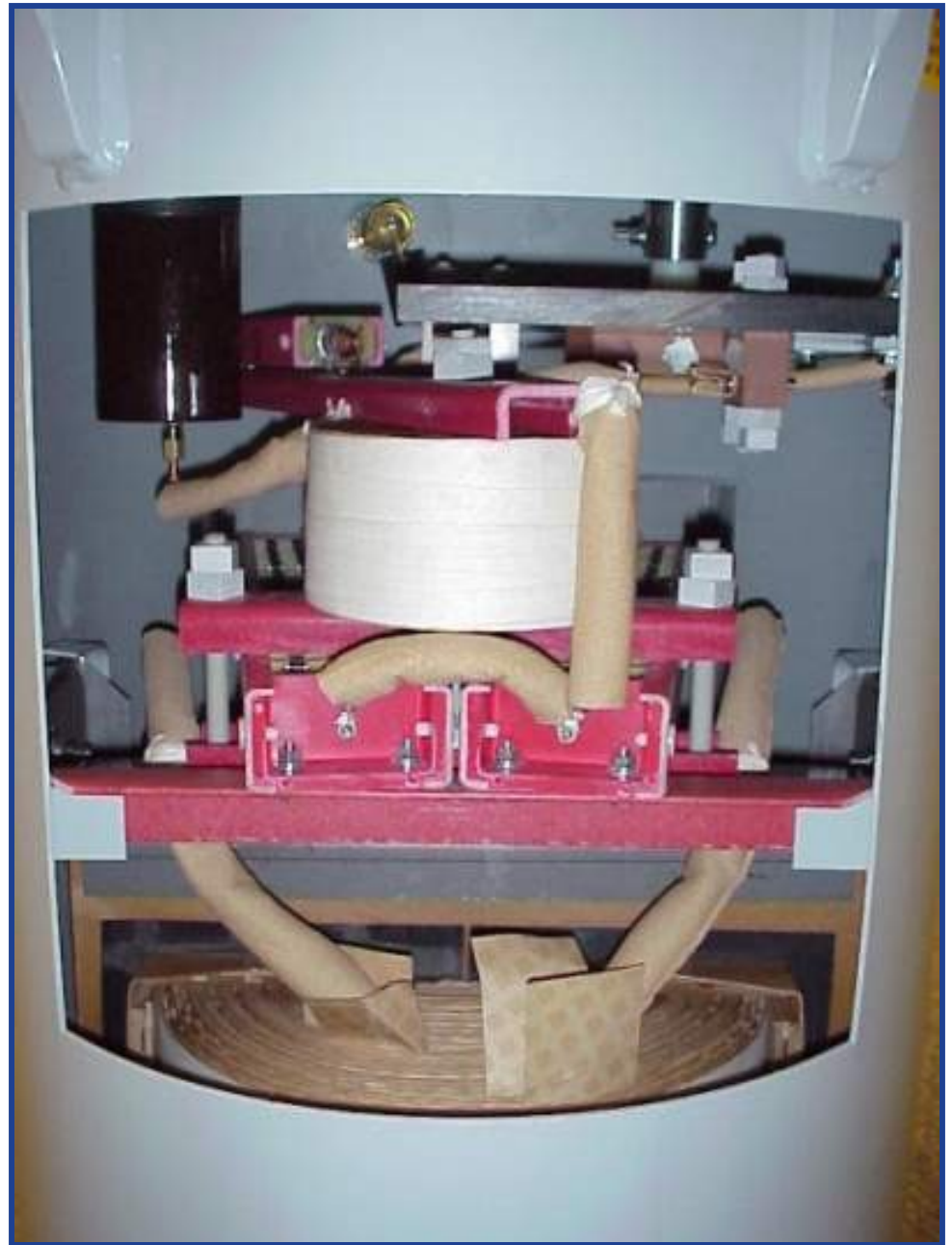

High Voltage Transformer



Diode Stack




T/R Set - Low Voltage Junction Box




Low Voltage Junction Box




T/R Nameplate

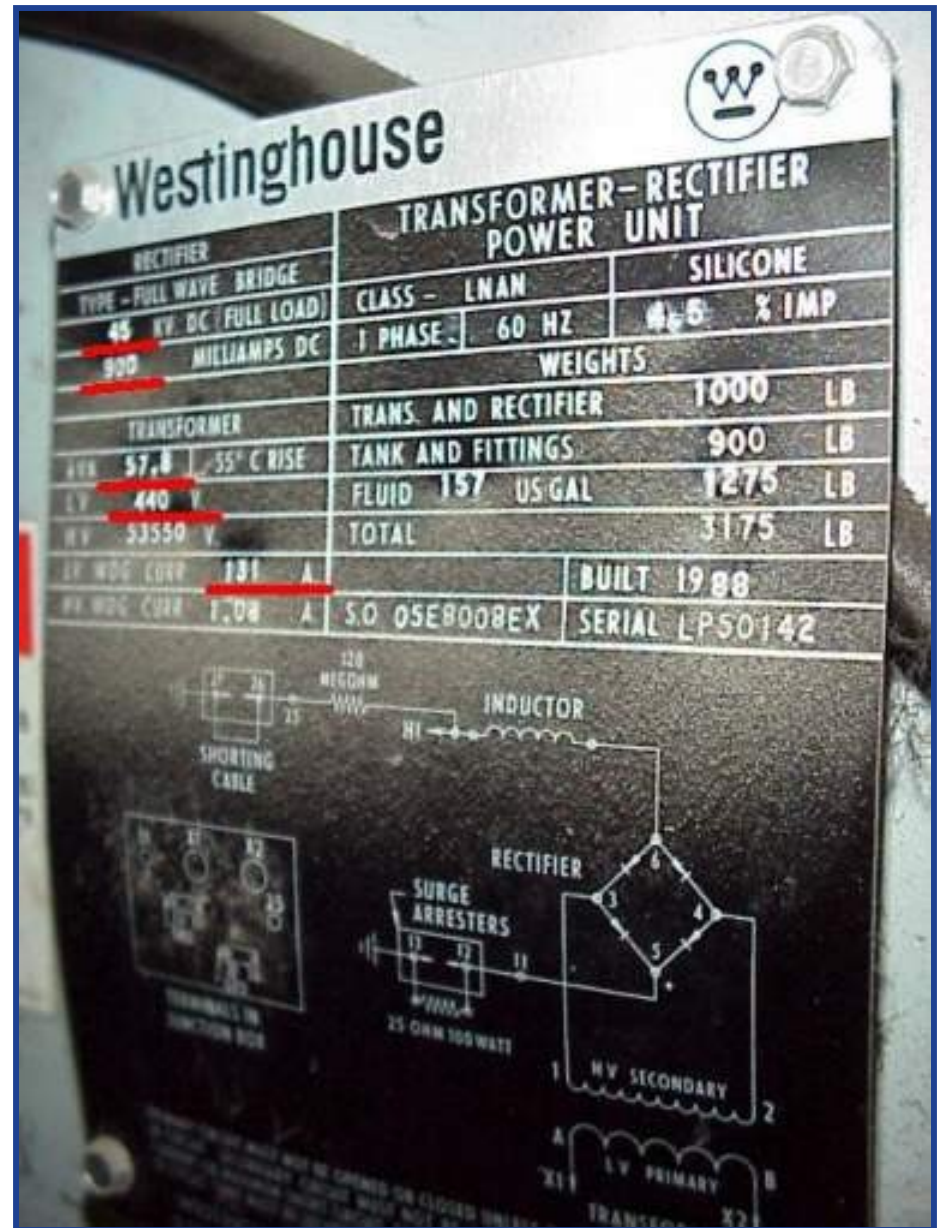


The KV Meter

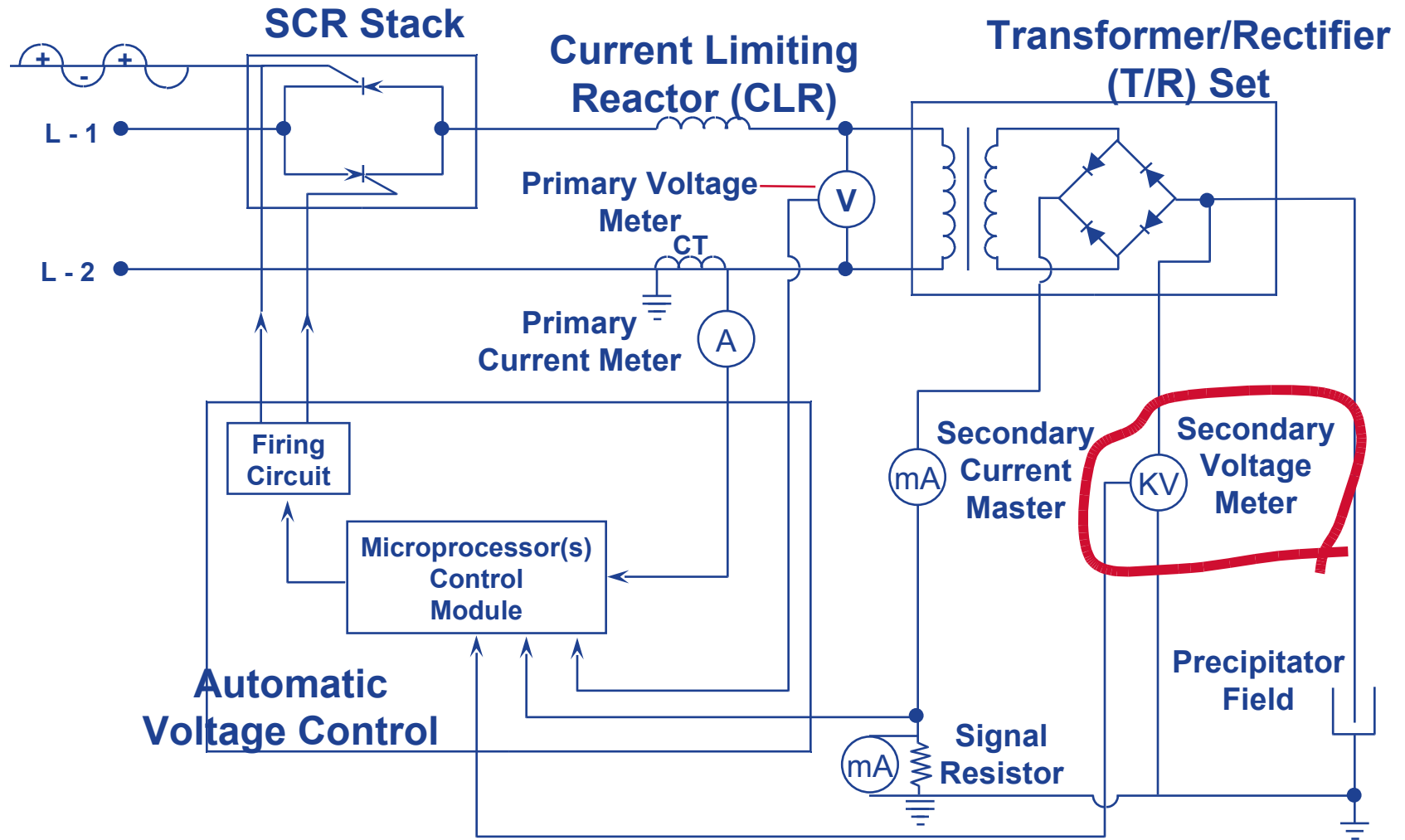


Voltage Divider

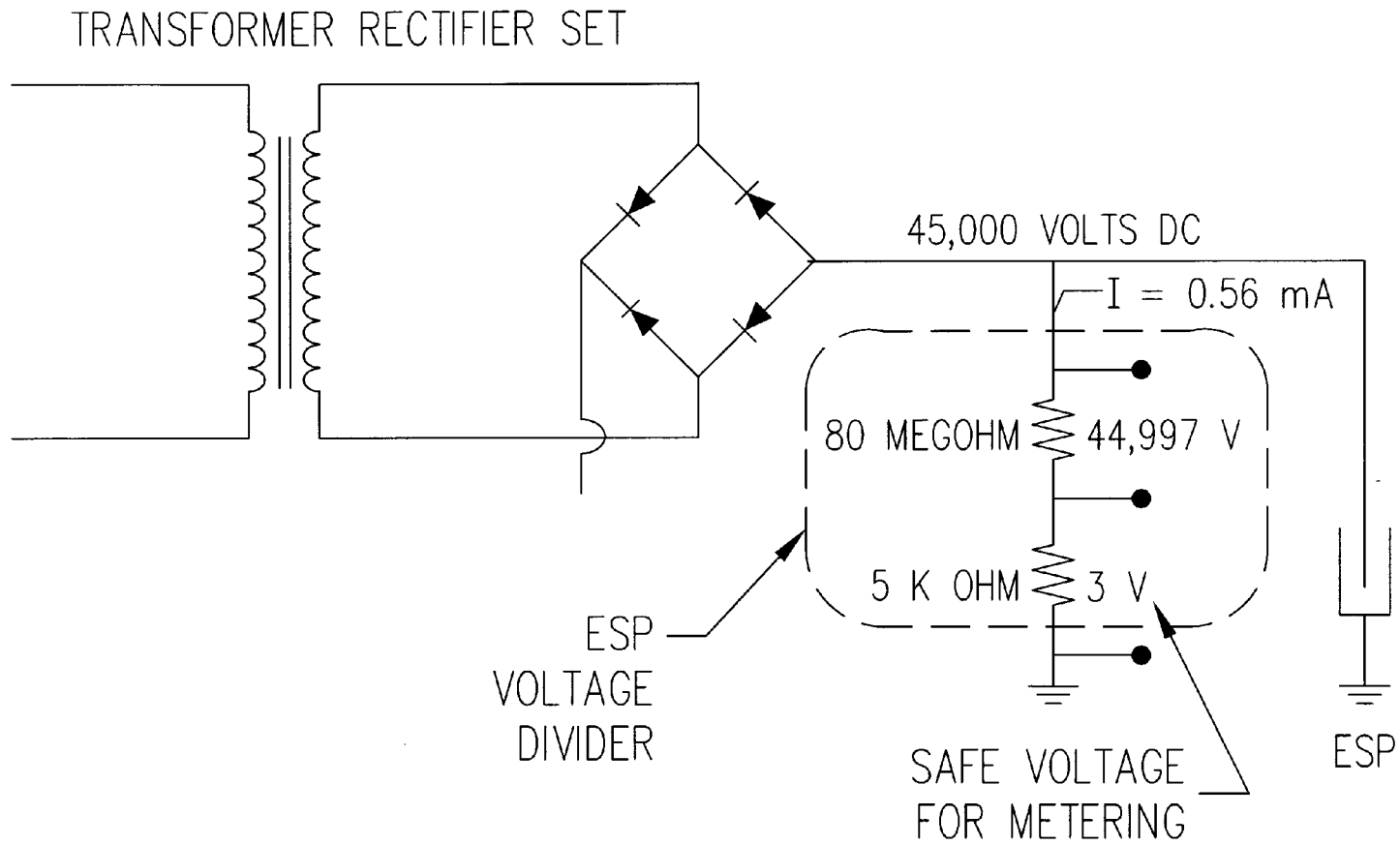


SCR'S

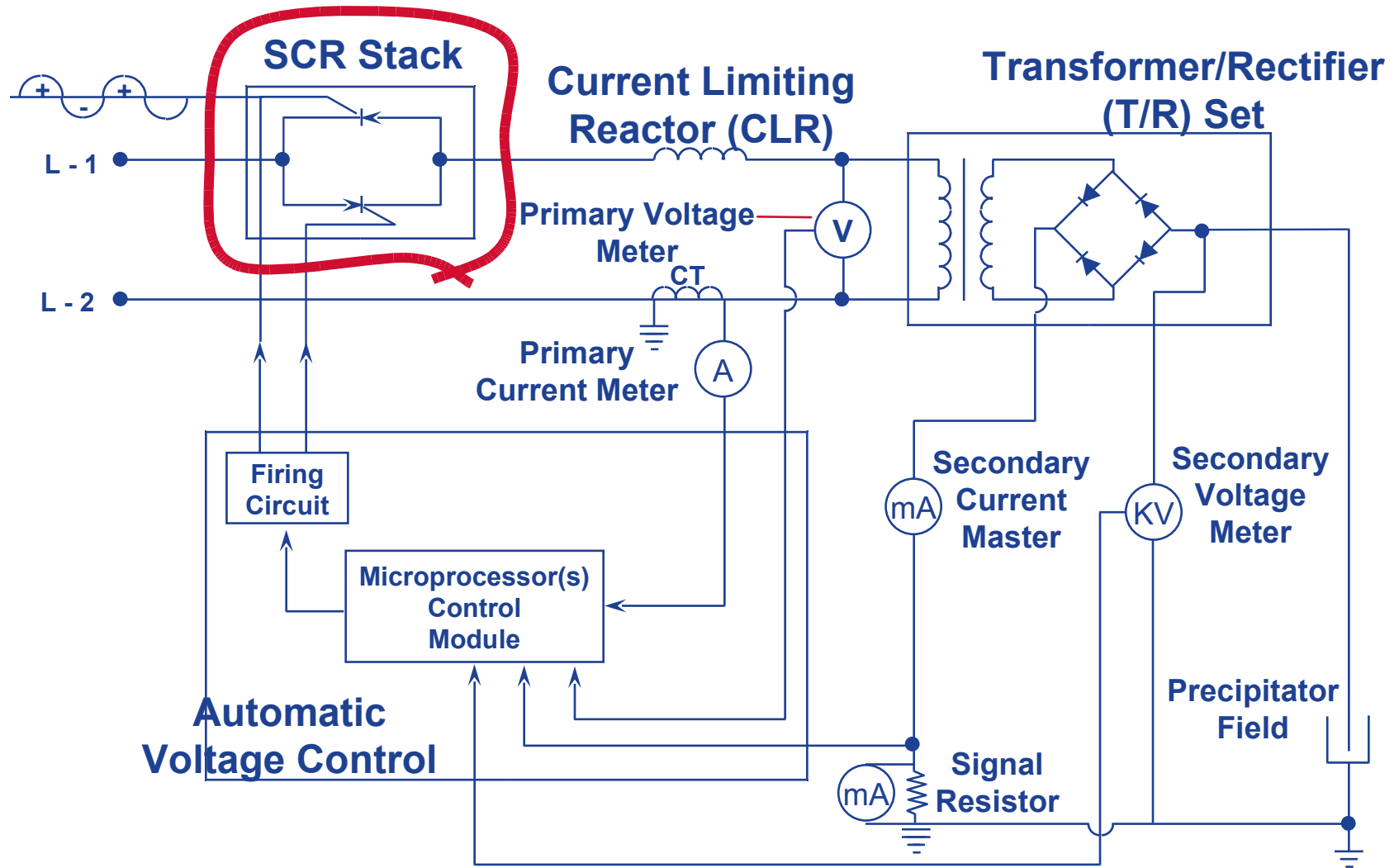


SCR

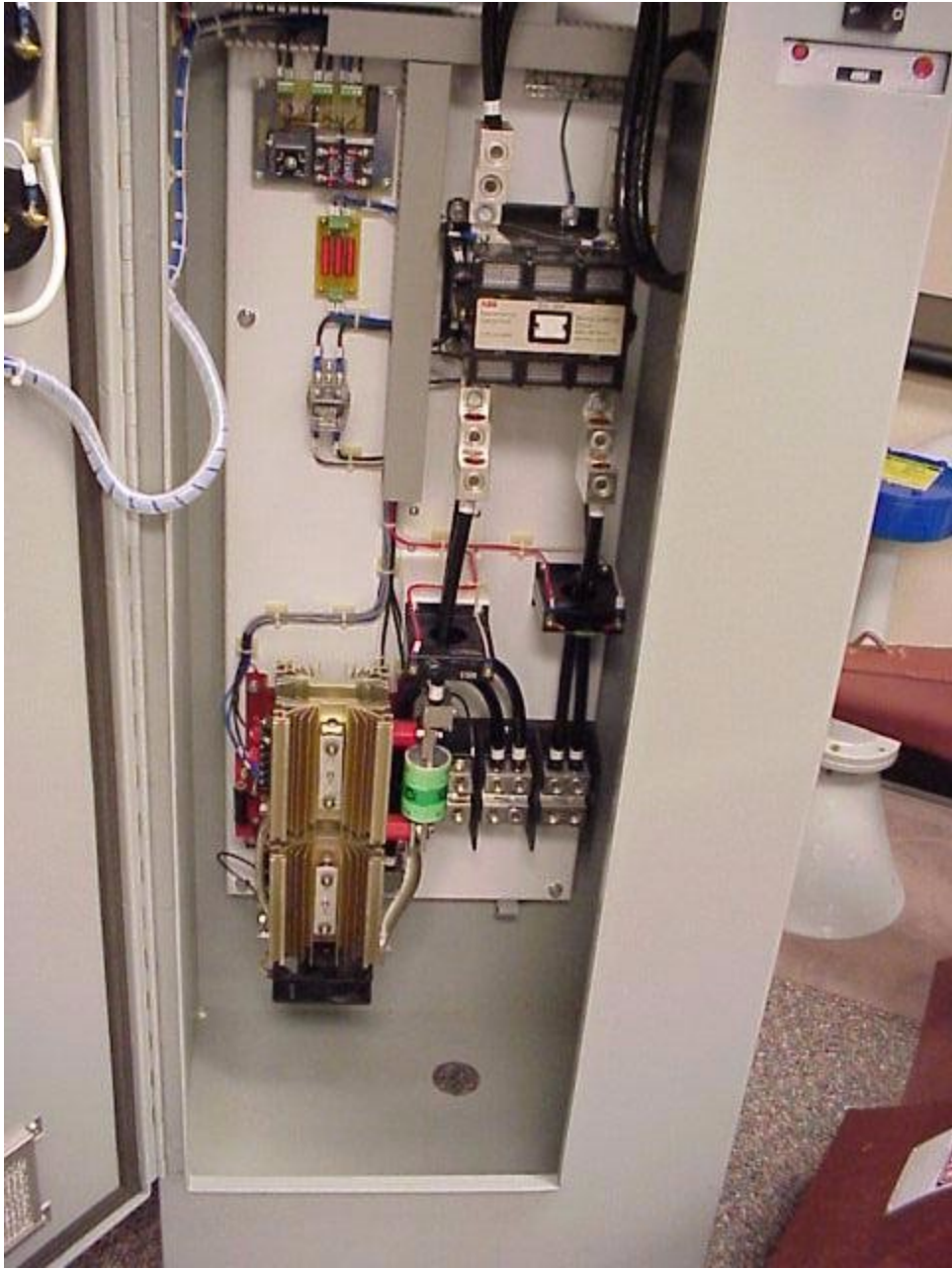

Typical Sine Wave

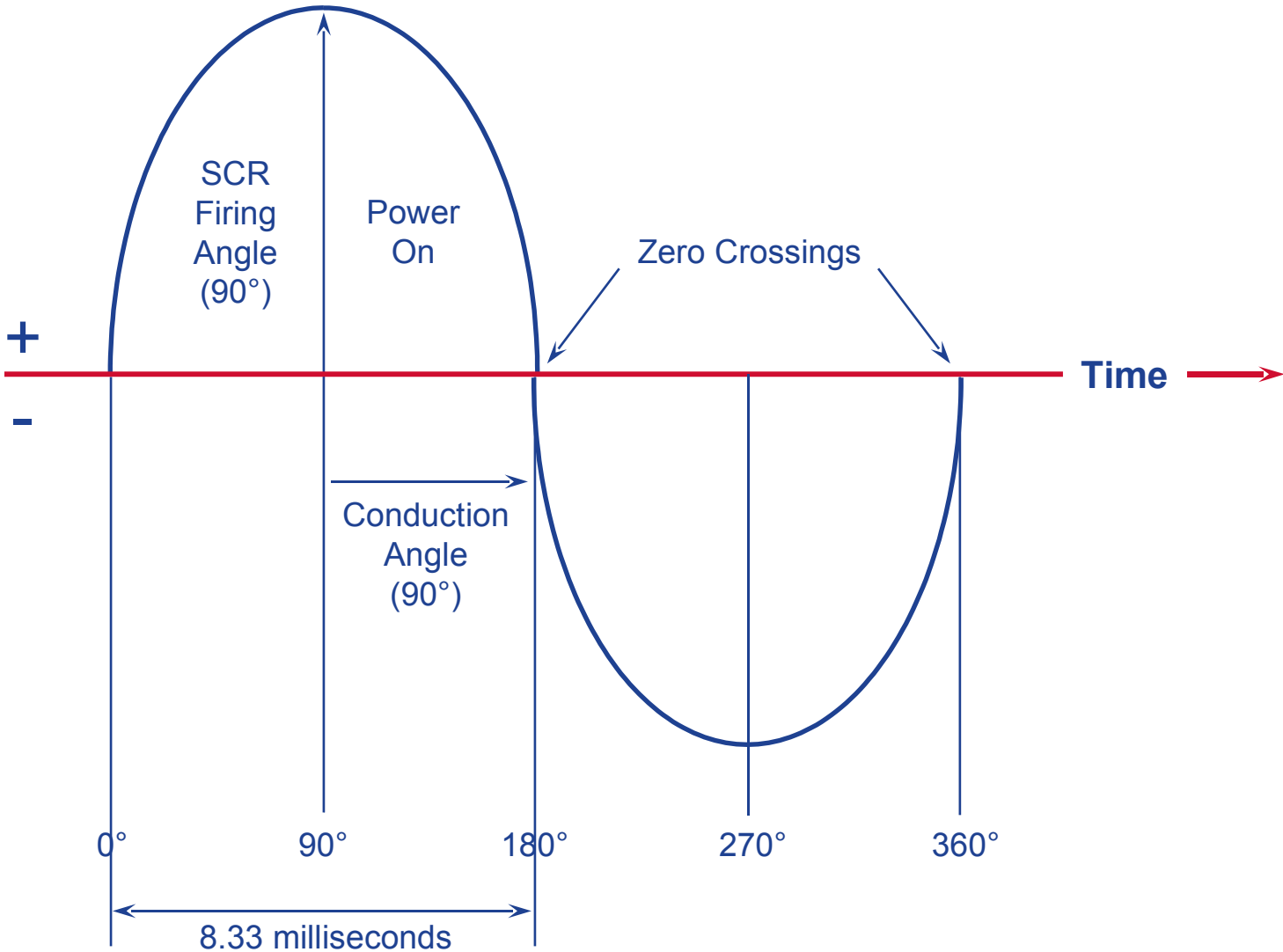


SCR: Low Voltage to T-R Set

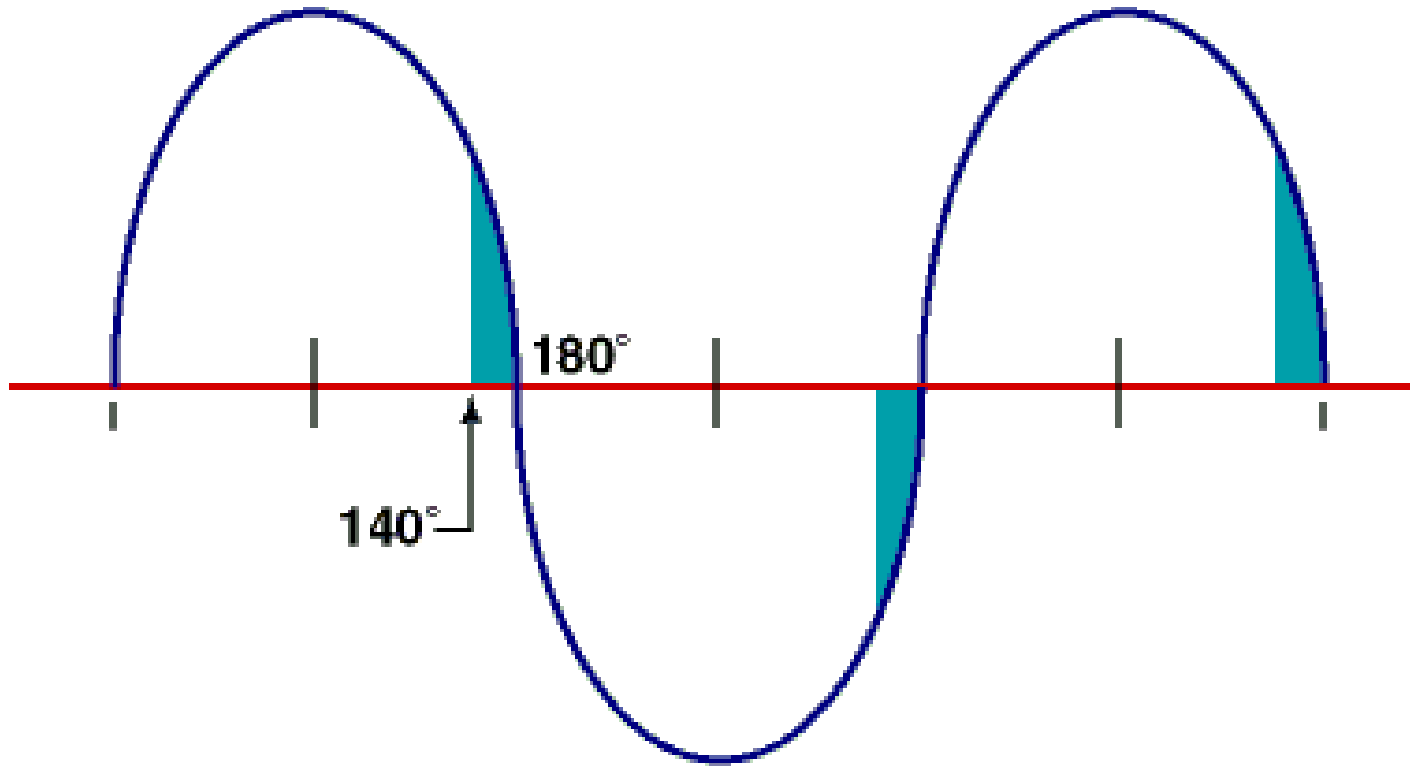


Firing Angle 140°
Conduction angle 40°

SCR: High Power to T-R Set

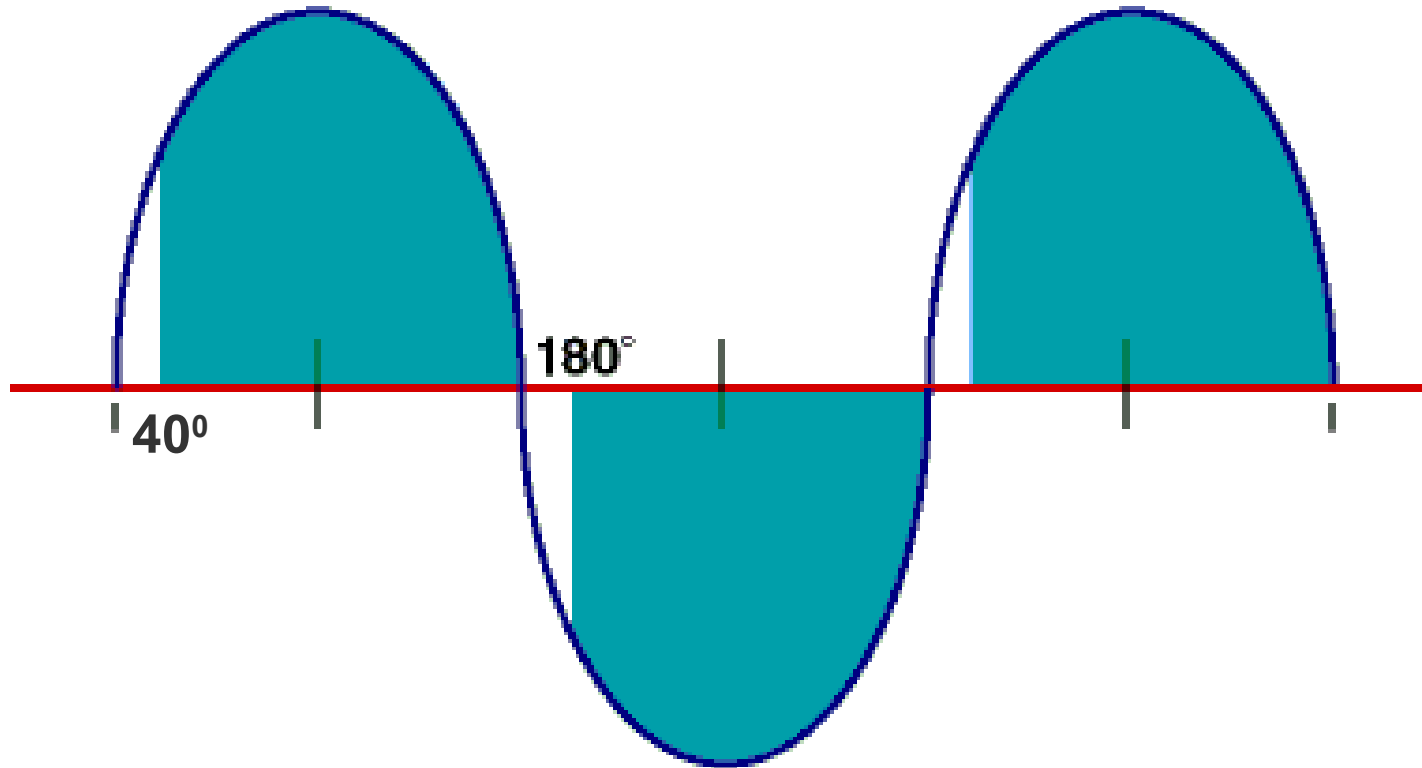

Firing Angle 40°
Conduction angle 140°

The CLR

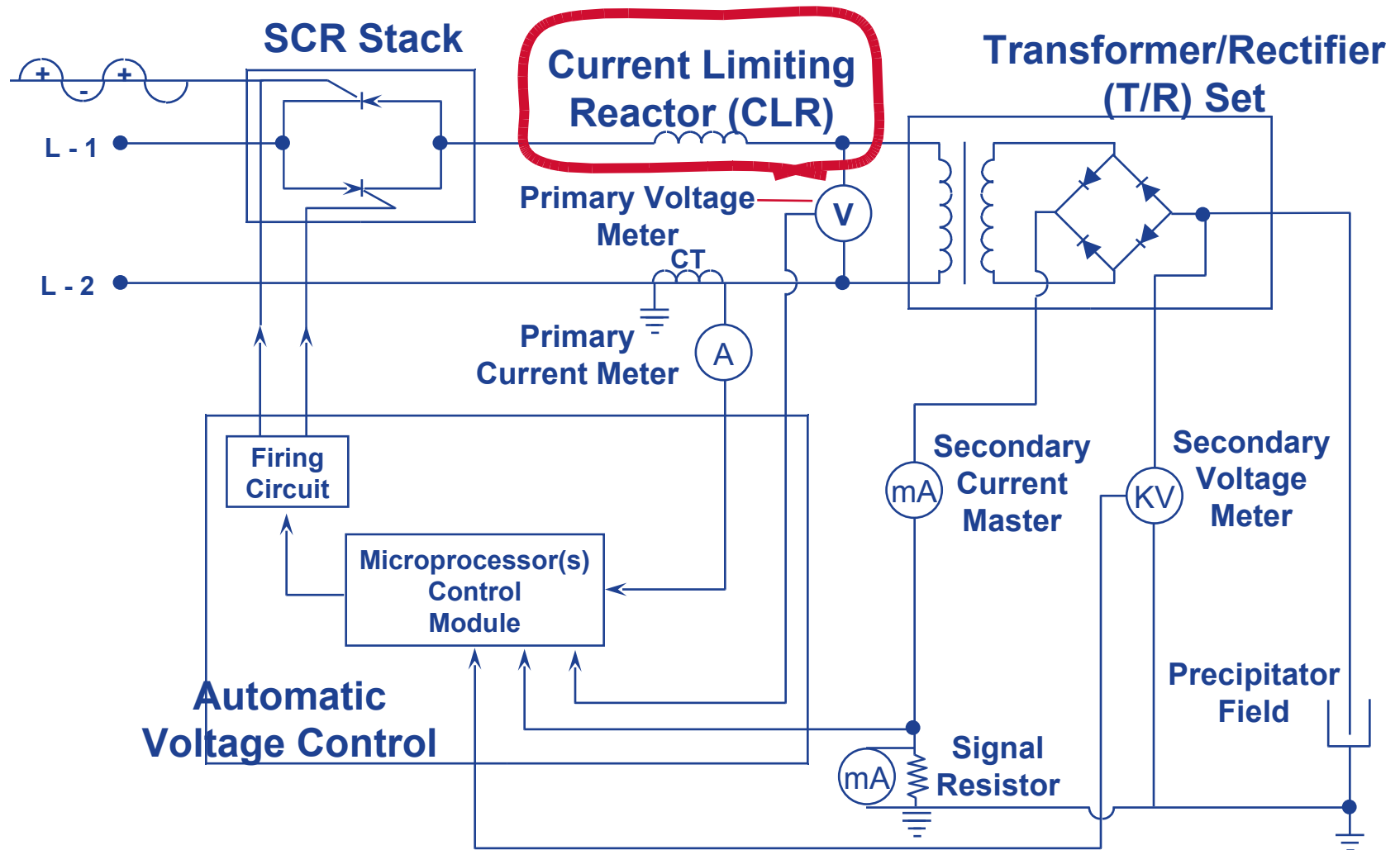

Current Limiting Reactor (CLR)



Current Limiting Reactor




Current Limiting Reactor at T-R Set



SCR's are why CLR's are Needed

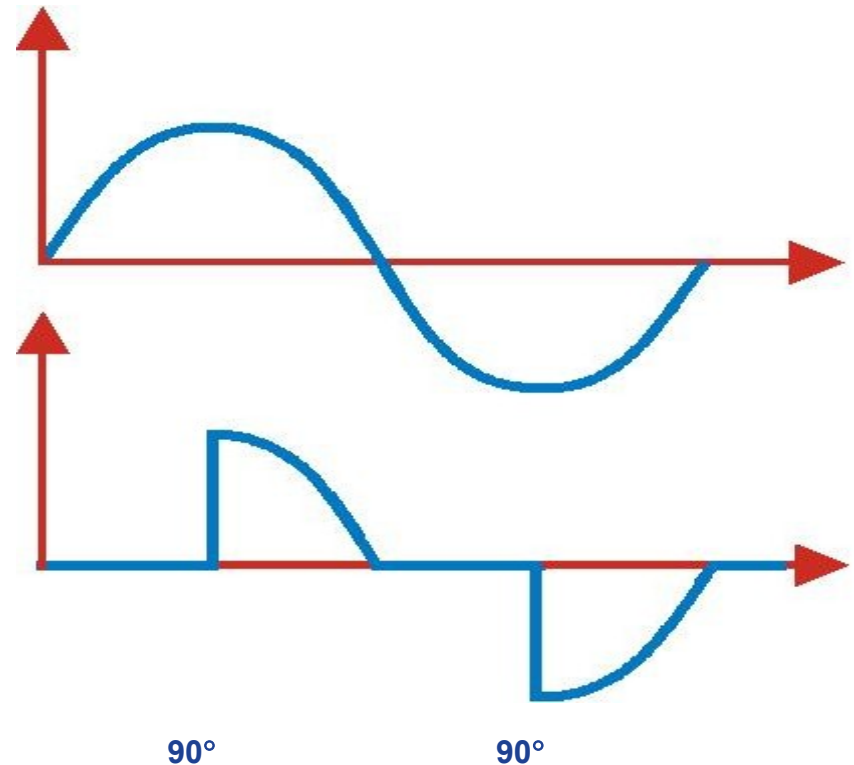
- The diagram would represent the waveform with the SCRs turning on at 90° .
- If this waveform were applied to the T/R set, very inefficient operation would occur.
- Output power from the T/R set would be greatly reduced.



Electrical Basics: CLR

To increase the efficiency of the T/R set, a device called a CLR (current limiting reactor) is used. A CLR is an inductor. Recall that the property of an inductor is to oppose a change in current. Because of this property, the shape of the current waveform is changed and it starts looking more like a sine


W ξ

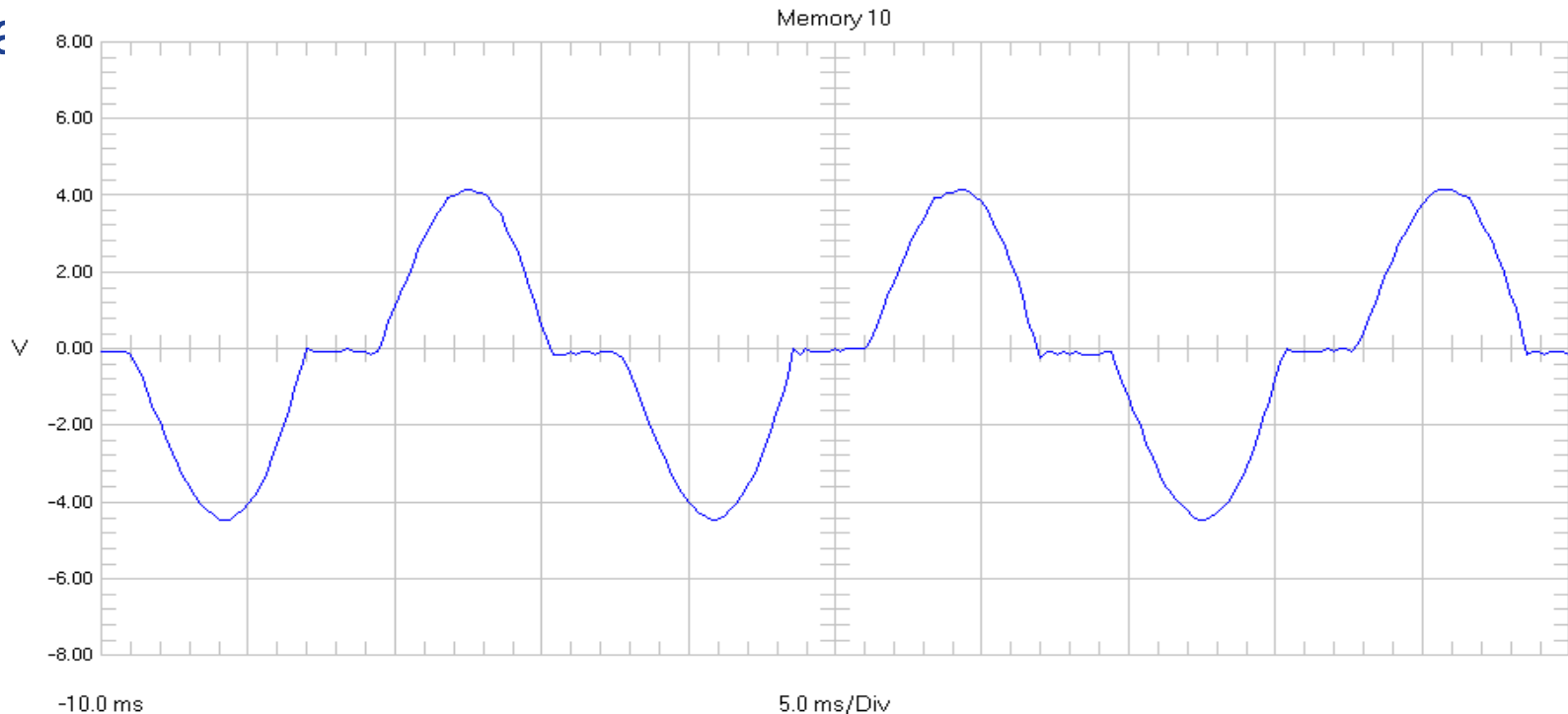

CLR Function

- Limit short circuit current
- Shape T/R secondary wave to be more sinusoidal
- Provide proper form factor
- Protect SCRs and T/R diodes from steep current rise
- Increase precipitator voltage and current
- Not to be confused with air core reactor

CLR – Waveform Changes with Impedance

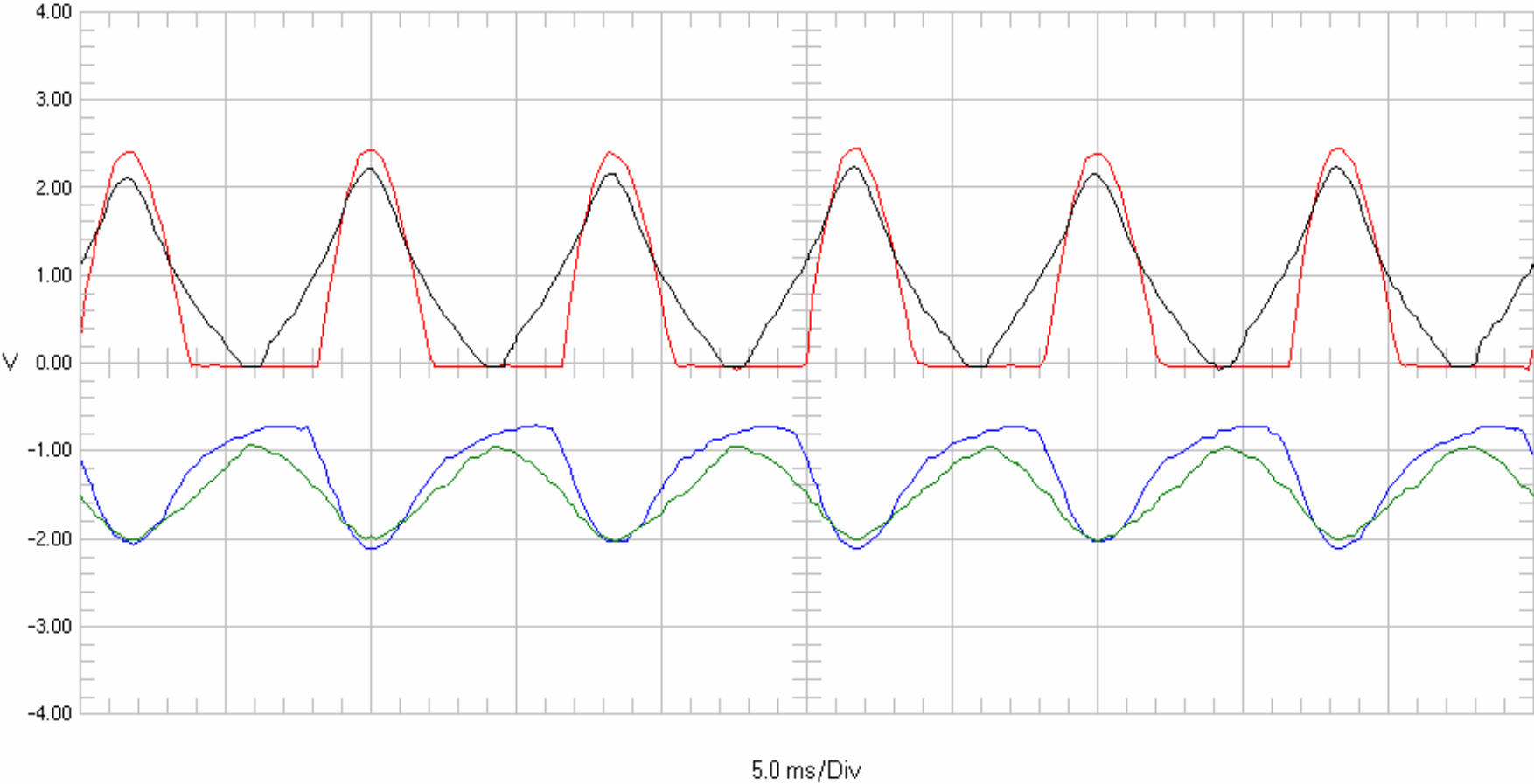

Proper CLR Sizes for Common T/R Sets

All T/R primaries are rated at 400V

PRI Current (Amps)	Sec. Current (mA)	Minimum (mH)
40	250	13.0
80	500	6.6
120	750	4.4
160	1000	3.3
200	1250	2.6
240	1500	2.2

Basic Troubleshooting

GE Energy



TR Nameplate Values (For this exercise)

Primary Current 160 Amps

Primary Voltage 480 Volts

Secondary Current 1200 mA

Secondary Voltage 45 kV

First Indication

160

480

1200

45

```
AMP      Volt      MA      KV      SCR      KW      S/M
160      045      1067    00.9    081      00      00
* Primary Current Limit *
* Run *
```

Second Indication

```
AMP      Volt      MA      KV      SCR      KW      S/M
160      045      1067    00.9    081      00      00
* Primary Under Voltage Alarm *
* Main Power Off *
```

Short

Close Clearance

160

480

1200

45

AMP	Volt	MA	KV	SCR	KW	S/M
009	110	0027	14.0	170	04	30
		* Spark *				
		* Run *				

Conductive Dust, Outlet Field

160

480

1200

45

AMP	Volt	MA	KV	SCR	KW	S/M
160	382	1177	32.1	081	38	00
* Primary Current Limit *						
* Run *						

Bad KV Return

160

480

1200

45

Amp	Volt	MA	KV	SCR	KW	S/M
160	382	1177	00.2	083	00	00
* Secondary Under Voltage Alarm *						
* Main Power Off *						

Open

160

480

1200

45

Amp	Volt	MA	KV	SCR	KW	S/M
000	452	0000	45.0	050	00	00
* Secondary Voltage Limit *						
* Run *						

Normal Running Condition

160

480

1200

45

AMP	Volt	MA	KV	SCR	KW	S/M
100	239	0584	29.9	100	17	30
		* Spark *				
		* Run *				

SCRs Not Firing

160

480

1200

45

```
Amp      Volt      MA      KV      SCR      KW      S/M
000      000      0000    00.0    016      00      00
* SCR Firing Angle Limit *
* Run *
```

Questions?

Thank You.



imagination at work